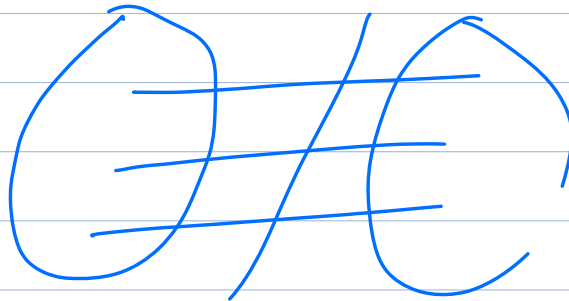


Announcements: Lecture on Nov 15 (Following Thu timetable)

: Syllabus : Nov 21 @ 2pm




(Network Topology)



$$Q_f \cdot i = 0 \quad \therefore A_i = 0$$

$$KVL: v = Q_f^T v_t$$

Example: Independent current sources

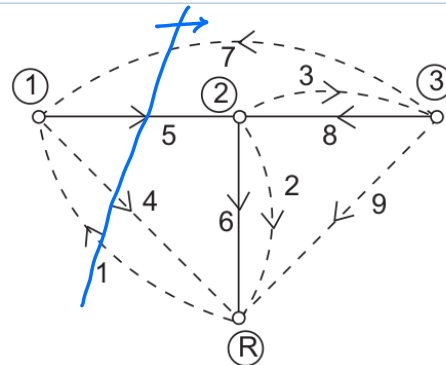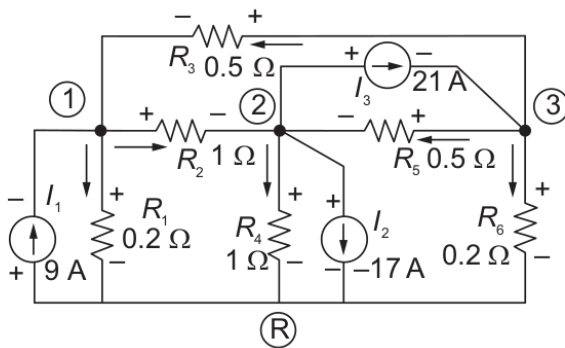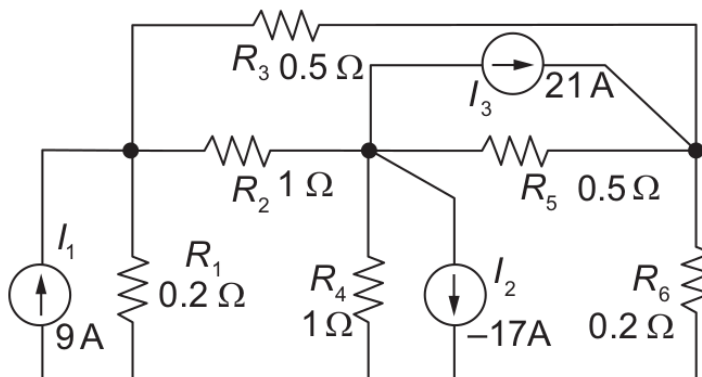

← 9 →  
1 2 3 4 5 6 7 8 9 7

$$Q_f = \begin{matrix} \leftarrow 5 \rightarrow \\ \leftarrow 6 \rightarrow \\ \leftarrow 7 \rightarrow \end{matrix} \left[ \begin{array}{ccc|cccc} -1 & 0 & 0 & 1 & 1 & 0 & -1 & 0 & 0 \\ & & & & & & & & \\ & & & & & & & & \\ & & & & & & & & \end{array} \right]$$

5, 7, 4, 1       $Q_{fg}$                        $Q_{fp}$

$$Q_f i = 0$$

$$\begin{bmatrix} Q_{fg} & Q_{fp} \end{bmatrix} \begin{bmatrix} i_g \\ i_p \end{bmatrix} = 0$$

$$i_g = \begin{bmatrix} 9 \\ -17 \\ 21 \end{bmatrix}$$

$$Q_{fg} i_g + Q_{fp} i_p = 0$$

$$i_p = Y_p \cdot V_p$$

↑  
admittance matrix

$$Y_p = \text{diag} \left( \begin{bmatrix} 5 & 0 \\ 0 & 0 \end{bmatrix} \right)$$

$$Q_{fg} i_g + Q_{fp} \cdot Y_p \cdot V_p = 0$$

KVL in terms of  $V$

$$V = Q_f^T V_t$$

$$\begin{bmatrix} V_g \\ V_p \end{bmatrix} = \begin{bmatrix} Q_{fg}^T \\ Q_{fp}^T \end{bmatrix} V_t$$

$$V_p = Q_{fp}^T V_t$$

$$Q_{fg} i_g + Q_{fp} y_p + Q_{fp}^T v_t = 0$$

$$\underline{v_t} = - [Q_{fp} y_p + Q_{fp}^T]^{-1} Q_{fg} i_g$$

## Tellegen's Theorem

Node voltage  $\Rightarrow$  branch voltage.

$$v = A^T v_n$$

↑  
branch voltage

↑  
node voltage

$$v^T i = (A^T v_n)^T i$$

$$= v_n^T \underbrace{(A i)}_0$$

inner product  
b/w branch  
voltage &  
branch currents

$$= 0,$$

$$\sum_{j=1}^b v_j i_j = 0$$

instantaneous power

" Total power delivered to all branches.  
at every instant is 0 "

✕ ————— Module 3 —————>

Module 2: Laplace transform

$$\begin{matrix} \mathcal{L}[f(t)] \\ F(s) \end{matrix} = \int_{0^-}^{\infty} f(t) e^{-st} dt.$$

Region of convergence (ROC)

→ Region in the  $s$ -plane where  $F(s)$  exists

1. Linearity

2.  $L \left[ \frac{d}{dt} f(t) \right]$

3.  $L \left[ \int_0^t f(t) \right]$

4.  $L [t f(t)]$

5. Initial & Final value theorem

$$F(s) \xrightarrow{L^{-1}} F(t)$$

Partial Fraction expansion

$$F(s) = \frac{P(s)}{Q(s)} \quad \begin{array}{l} \text{order}(P) = m \\ \text{order}(Q) = n \end{array}$$


$$m < n$$

$$= \frac{a_0 s^m + a_1 s^{m-1} + \dots + a_m}{b_0 s^n + b_1 s^{n-1} + \dots + b_n}$$

$$= \frac{a_0}{b_0} \frac{(s - z_1)(s - z_2) \dots (s - z_m)}{(s - p_1)(s - p_2) \dots (s - p_n)}$$

$z_i$ 's : Zeros of  $F(s)$


$p_i$ 's : Poles of  $F(s)$

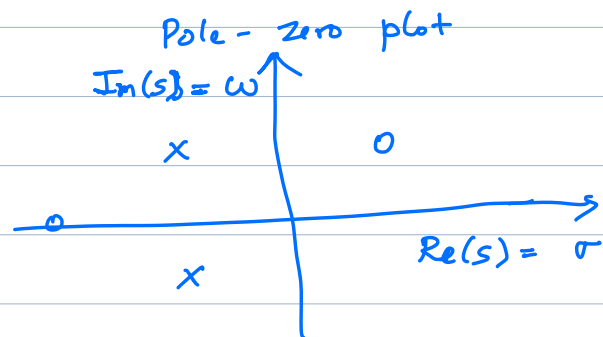

Example:  $F(s) = \frac{3(s+4)}{s^2 + 2s + 5}$

Poles:  $-1 \pm 2j$

Zeros:  $-4, \infty$

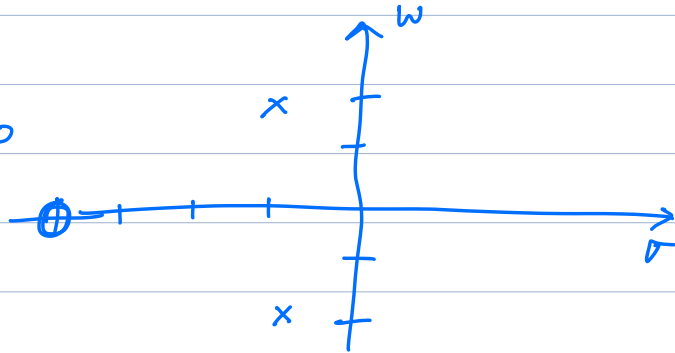

$s \rightarrow \infty$

$$F(s) = \frac{3 \cdot s}{s^2} = 3/s = 0$$

$m < n$   $n-m$  zeros at infinity

$m > n$   $m-n$  poles at infinity

Multiplicity of Poles & Zeros  $F(s) = \frac{1}{(s+a)^2}$

$F(s)$  has a pole at  $s = -a$   
with a multiplicity of 2.

Frequency response  $F(j\omega)$  from  $F(s)$

$$F(j\omega) = F(s) \Big|_{s = j\omega / \sigma = 0}$$