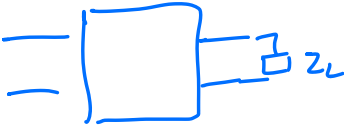



Last class



$$* Z_1 = Z_{11} - \frac{Z_{12} Z_{21}}{Z_L + Z_{22}}$$



$$Z_2 = Z_{22} - \frac{Z_{12} Z_{21}}{Z_L + Z_{11}}$$

$$Z_{10} = \frac{A}{C}$$


$$Z_{1s} = \frac{B}{D}$$

$$Z_{20} = \frac{D}{C}$$


$$Z_{2s} = \frac{B}{A}$$

Image Parameters (Reciprocal N/w)

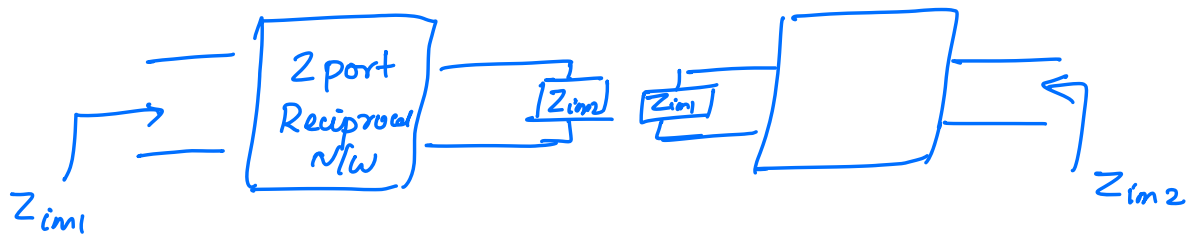
Z_{im1} Z_{im2} r
 Image impedances Image transfer constant



Example:
 (16.8.1 insk)

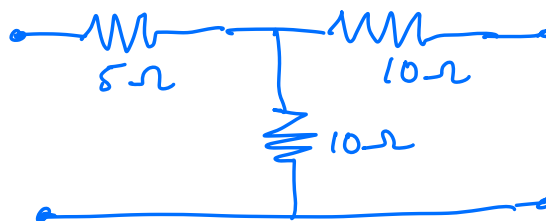

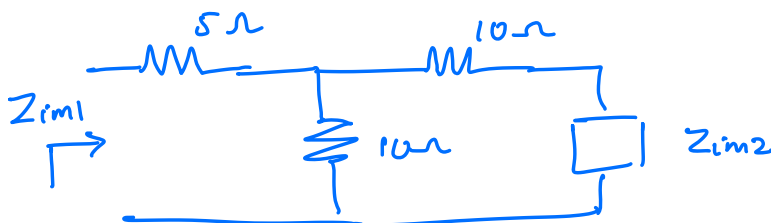
$$Z = \begin{pmatrix} 15 & 10 \\ 10 & 20 \end{pmatrix}$$



$$Z_{im1} = 5 + 10 \parallel (10 + Z_{im2})$$

$$Z_{im1} = 5 + 10 \left(\frac{10 + Z_{im2}}{20 + Z_{im2}} \right)$$
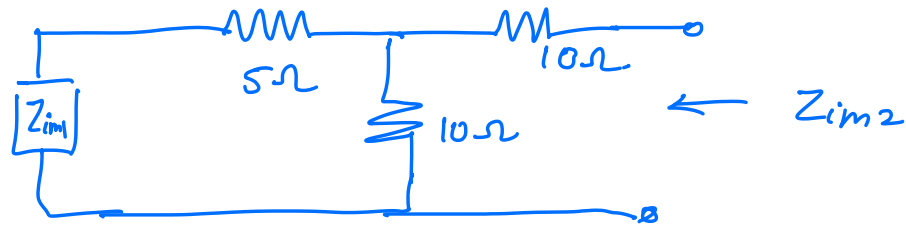
$$Z_{im1} (20 + Z_{im2}) = 200 + 15 Z_{im2} \quad -(1)$$



$$\begin{aligned} Z_{im2} &= 10 + 10 \parallel (5 + Z_{im1}) \\ &= 10 + 10 \frac{(5 + Z_{im1})}{15 + Z_{im1}} \end{aligned}$$


$$Z_{im2} (15 + Z_{im1}) = 200 + 20 Z_{im1} \quad -(2)$$

(1) & (2)

$$Z_{im1} = 12.25 \Omega$$

$$Z_{im2} = 16.33 \Omega //$$


Image impedance in terms of Transmission parameters

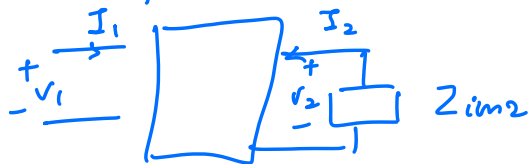

$$Z_{im1} = \frac{V_1}{I_1}$$

$$\left. \begin{aligned} V_1 &= A V_2 + B (-I_2) \\ I_1 &= C V_2 + D (-I_2) \end{aligned} \right\}$$

$V_2 = -I_2 Z_{im2}$ *

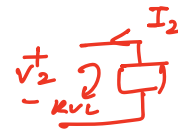

$$I_1 = C Z_{im2} (-I_2) + D (-I_2)$$


$$-I_2 = \frac{I_1}{C Z_{im2} + D}$$

$$V_1 = A (-I_2) Z_{im2} + B (-I_2)$$

$$V_1 = (A Z_{im2} + B) (-I_2)$$

$$V_1 = \frac{(A Z_{im2} + B)}{C Z_{im2} + D} I_1$$
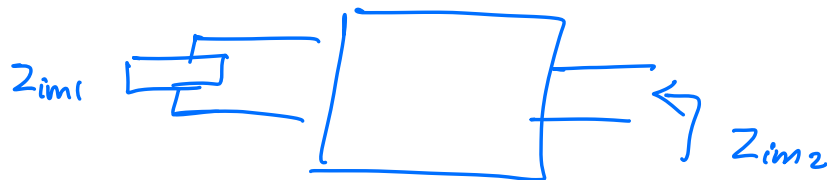
$$Z_{im1} = \frac{V_1}{I_1} = \frac{A Z_{im2} + B}{C Z_{im2} + D} \quad (1)$$



$$Z_{im2} = \frac{D Z_{im1} + B}{C Z_{im1} + A} \quad (2)$$

$$Z_{im1} = \sqrt{\frac{AB}{CD}} \quad Z_{im2} = \sqrt{\frac{DB}{CA}} \quad \left. \begin{array}{l} \text{Skip the step} \\ \text{of solving (1)} \\ \text{+ (2)} \end{array} \right\}$$

$$\det \begin{pmatrix} A & B \\ C & D \end{pmatrix} = 1 \quad (*) \quad (\text{Reciprocity})$$

$$Z_{10} = \frac{A}{C}$$

$$Z_{20} = \frac{D}{C}$$

$$Z_{1S} = \frac{B}{D}$$

$$Z_{2S} = \frac{B}{A}$$

$$Z_{im1} = \sqrt{Z_{10} Z_{1S}}$$

$$Z_{im2} = \sqrt{Z_{20} Z_{2S}}$$


Special case: Network is reciprocal and symmetric

$$\begin{array}{l} Z_{10} = Z_{20} = A/C \\ Z_{1S} = Z_{2S} = B/A \end{array} \quad \left\{ \begin{array}{l} \det \begin{pmatrix} A & B \\ C & D \end{pmatrix} = 1 \\ A = D \end{array} \right. \quad \begin{array}{l} \rightarrow Z_{oc} \\ \rightarrow Z_{sc} \end{array}$$

$$Z_{im1} = Z_{im2} = Z_0 (Z_c) = \sqrt{\frac{B}{C}}$$

↑
Characteristic impedance.

Image transfer constant (γ)

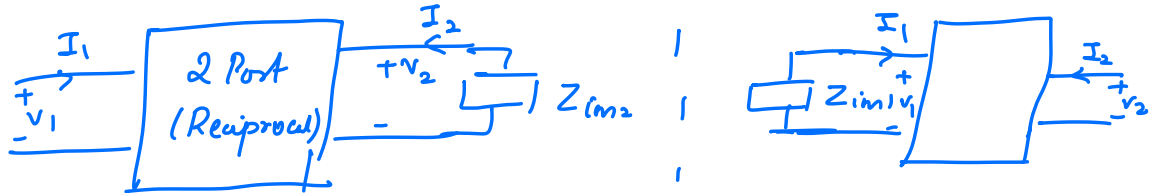

$$e^{\gamma} = \sqrt{\frac{V_1}{V_2} \frac{I_1}{(-I_2)}} \quad , \quad e^{\gamma} = \sqrt{\frac{V_2}{V_1} \frac{I_2}{(-I_1)}}$$

In terms of transmission parameters.

$$V_1 = A V_2 + B (-I_2)$$

$$I_1 = C V_2 + D (-I_2)$$

$$V_2 = -Z_{im2} I_2$$

$$I_1 = C (-Z_{im2} I_2) + D (-I_2)$$

$$\frac{I_1}{-I_2} = D + C \cdot Z_{im2} \quad Z_{im2} (*)$$

$$= D + C \cdot \sqrt{\frac{DB}{CA}}$$

$$= D + \sqrt{\frac{BCD}{A}} = D + \frac{\sqrt{ABCD}}{A}$$

$$V_1 = A \cdot V_2 + B \frac{V_2}{Z_{im2}}$$

$$\frac{V_1}{V_2} = A + \frac{B}{Z_{im2}} = A + \frac{B}{\sqrt{\frac{DB}{CA}}}$$

$$= A + \sqrt{\frac{ABC}{D}} = A + \frac{\sqrt{ABCD}}{D}$$

$$e^r = \sqrt{\begin{pmatrix} V_1 \\ V_2 \end{pmatrix} \begin{pmatrix} I_1 \\ -I_2 \end{pmatrix}}$$

$$(e^r)^2 = \left(A + \frac{\sqrt{ABCD}}{D} \right) \left(D + \frac{\sqrt{ABCD}}{A} \right)$$

$$= AD + \frac{ABCD}{AD} + 2\sqrt{ABCD}$$

$$= AD + BC + 2\sqrt{ABCD}$$

$$= (\sqrt{AD} + \sqrt{BC})^2$$

$$e^r = \sqrt{AD} + \sqrt{BC}$$

$$\det \begin{pmatrix} A & B \\ C & D \end{pmatrix} = 1 \quad \begin{matrix} AD - BC = 1 \\ BC = AD - 1 \end{matrix}$$

$$e^r = \sqrt{AD} + \sqrt{AD - 1}$$

Special Case: Reciprocal & Symmetric

$$e^r = \sqrt{AD} + \sqrt{BC}$$

$$= A + \sqrt{BC}$$

$$= A + \frac{B}{\sqrt{\frac{B}{C}}} = A + \frac{B}{Z_0} //$$

$$\frac{V_1}{V_2} = A + \frac{\sqrt{ABCD}}{D} = A + \sqrt{B/C} \quad \checkmark$$

$$(A = D) \quad = e^r //$$

$$\frac{I_1}{-I_2} = D + \frac{\sqrt{ABCD}}{A} = A + \sqrt{B/C}$$

$$(A = D) \quad = e^r //$$

$$\frac{V_1}{V_2} = \frac{I_1}{-I_2} = e^r //$$