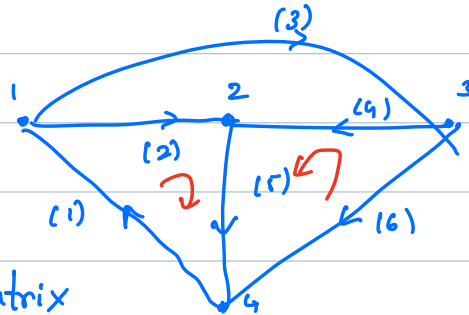


Last class: (i) Incidence matrix

(ii) Nodal Analysis

[Tutorial] - No tutorial this week.

Tutorial sessions are "back" to  
Wed 5-6 pm.




← Circuit Matrix


$$\begin{matrix} B \\ \uparrow \\ a \\ \uparrow \\ all \end{matrix} = \begin{matrix} Loop 1 \\ Loop 2 \\ \vdots \\ Loop l \end{matrix} \begin{bmatrix} (1) & (2) & (3) & (4) & (5) & (6) \\ 1 & 1 & 0 & 0 & 1 & 0 \end{bmatrix} \begin{matrix} \\ \\ \\ Loop l \end{matrix}$$

$$b_{ij} = \begin{cases} 0 & , \text{ if the loop } i \text{ doesn't contain branch } j \\ 1 & , \text{ branch same direction as loop } \\ -1 & , \text{ opposite direction. } \end{cases}$$

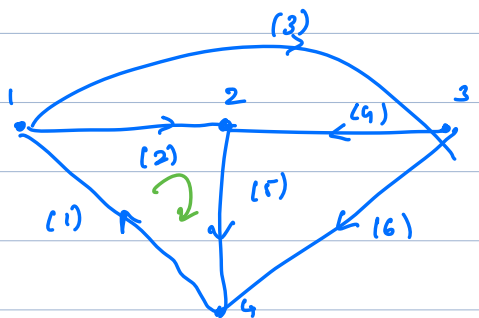$b_{ij}$   
 $\uparrow \quad \uparrow$   
 $i^{th} \text{ loop} \quad j^{th} \text{ branch}$



b branches

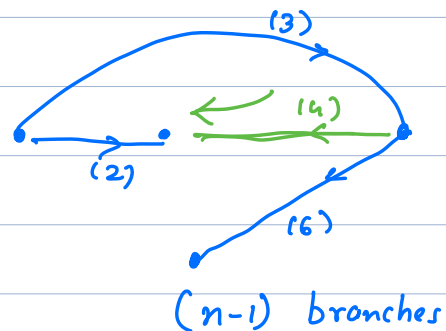

(n-1) branches

Fundamental circuit matrix ( $B_f$ )  $\begin{pmatrix} b - (n-1) \\ \text{loops} \end{pmatrix}$

$$B_f = \begin{matrix} f-c-1 \\ f-c-2 \\ f-c-3 \end{matrix} \begin{bmatrix} (1) & (2) & (3) & (4) & (5) & (6) \\ 0 & -1 & 1 & 1 & 0 & 0 \end{bmatrix} \rightarrow \begin{matrix} \text{Circuit obtained by} \\ \text{putting one of the} \\ \text{links in the tree} \\ \text{(+ circuit)} \end{matrix}$$

$b - (n-1)$

Properties of  $B_f$

$$B_f = \begin{matrix} (2) & (3) & (6) & (4) & (1) & (5) \\ \begin{bmatrix} & & & 1 & 0 & 0 \\ & & & 0 & 1 & 0 \\ & & & 0 & 0 & 1 \end{bmatrix} \end{matrix} \begin{matrix} f-c-1 (4) \\ f-c-2 (1) \\ f-c-3 (5) \end{matrix}$$

$\leftarrow \text{tree} \rightarrow \quad \leftarrow \text{links} \rightarrow$

$B_{ft} \quad B_{fl} = I_{b-(n-1)}$

$$\text{rank}(B_{fl}) = b - (n-1)$$

$$\text{rank}(B_f) \geq b - (n-1)$$

Prop (Proof skip)  $\text{rank}(B_f) = b - (n-1)$

KVL equations:

$$v(t) = [v_{(1)}(t) \ v_{(2)}(t) \ \dots \ v_{(b)}(t)]$$

$\uparrow$  branch voltages

$$B_f \cdot v(t) = 0 \quad [\text{KVL in matrix form}].$$

$B_a \cdot v(t) = 0$


$$\left[ \leftarrow \text{loop 1} \rightarrow \right] \left[ \begin{matrix} \uparrow \\ \downarrow \end{matrix} \right] = 0$$

$\uparrow$  branch voltages


KCL equations :  $A_i(t) = 0$

in terms of B matrix?

[ Relation b/w A & B matrix ]

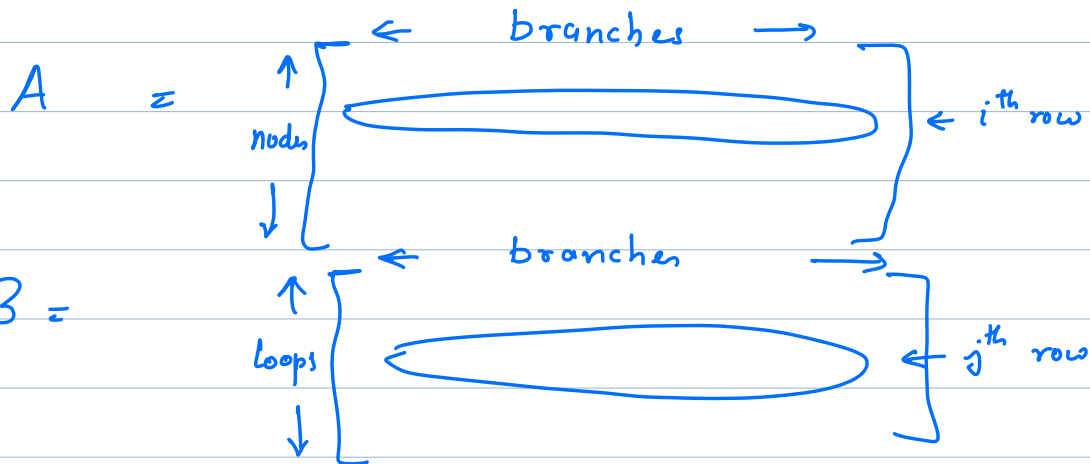

$$A_i^T B_j$$

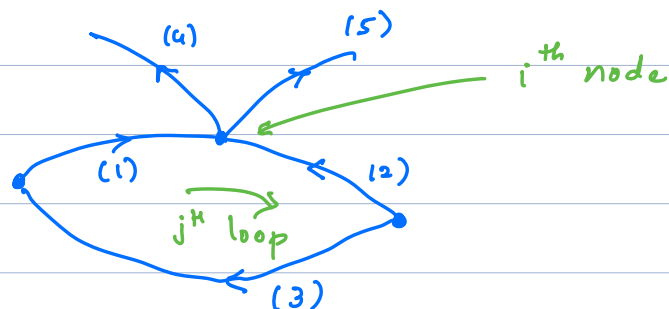

$$A_i = \begin{bmatrix} (1) & (2) & (3) & (4) & (5) \\ -1 & -1 & 0 & 1 & 1 \end{bmatrix}$$


$$B_j = \begin{bmatrix} 1 & -1 & 1 & 0 & 0 \end{bmatrix}$$

$$A_i B_j^T = 0 //$$

Key idea: Any loop, for any node there would be 2 branches

All other branches are either not incident at that node or

not in the loop

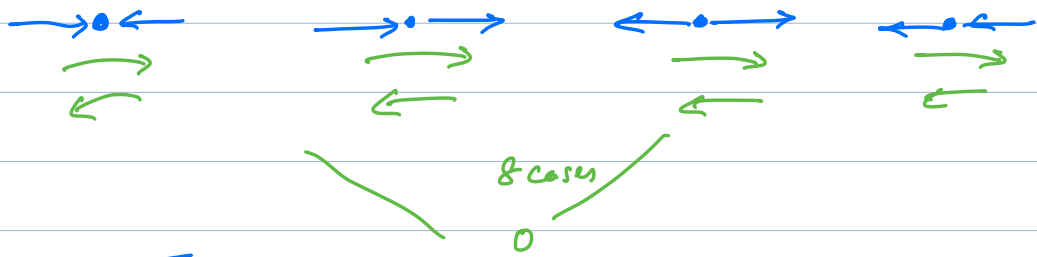

$$A_i B_j^T = 0$$

Property:

$$A B^T = 0$$

$$A_a B_a^T = 0$$

$$A B_f^T = 0$$

Orthogonality  
relation  
between

$A$  &  $B$  matrix

$$\dim(A) = (n-1) \times b$$

$$\dim(B_f) = b - (n-1) \times b$$

$$B_f = \begin{bmatrix} B_{ft} & B_{fe} \end{bmatrix}$$

↓

$$= \begin{bmatrix} B_{ft} & I \end{bmatrix}^T$$

$$A = \begin{bmatrix} A_t & A_e \end{bmatrix}$$

$$\begin{bmatrix} A_t & A_e \end{bmatrix} \begin{bmatrix} B_{ft}^T \\ I \end{bmatrix} = 0$$

$$A_t B_{ft}^T + A_e = 0$$

$$B_{ft} = - (A_t^{-1} A_e)^T //$$

KCL using B matrix

$$A i(t) = 0$$

$$\begin{bmatrix} A_t & A_e \end{bmatrix} \begin{bmatrix} i_t \\ i_e \end{bmatrix} = 0$$

$$A_t i_t + A_e i_e = 0$$

$$i_t = - \boxed{A_t^{-1} A_e} i_e$$

$$= B_{ft}^T i_e //$$