

Announcements : - Tutorial Sheet on 2 port posted
 - Tutorial class on Wed

Last Week - 2 port parameters (Z, Y, H, G, T)

Transmission Parameters (ABCD)

$$V_1 = A V_2 + B (-I_2)$$

$$I_1 = C V_2 + D (-I_2)$$

Inverse Transmission Parameters (T')

$$\begin{bmatrix} V_2 = A' V_1 + B' (-I_1) \\ I_2 = C' V_1 + D' (-I_1) \end{bmatrix}$$



$$A' = \left. \frac{V_2}{V_1} \right|_{I_1=0} \quad (\text{Forward voltage ratio})$$

$$C' = \left. \frac{I_2}{V_1} \right|_{I_1=0} \quad \text{o/p ckt transfer admittance}$$

$$B' = \left. \frac{V_2}{-I_1} \right|_{V_1=0} \quad \text{short ckt transfer impedance}$$

$$D' = \left. \frac{I_2}{-I_1} \right|_{V_1=0} \quad (\text{Forward current ratio})$$



$$\begin{cases} Z = Y^{-1} \\ H = G^{-1} \\ T = (T')^{-1} \end{cases}$$

Z-parameter in terms of transmission parameters.

$$\begin{array}{l} V_1 = A V_2 + B(-I_2) \\ I_1 = C V_2 + D(-I_2) \end{array} \quad \left| \quad \begin{array}{l} V_1 = Z_{11} I_1 + Z_{12} I_2 \\ V_2 = Z_{21} I_1 + Z_{22} I_2 \end{array} \right.$$

$$C V_2 = I_1 + D I_2$$

$$V_2 = \frac{1}{C} I_1 + \frac{D}{C} I_2$$

$$Z_{21} = \frac{1}{C} \quad Z_{22} = \frac{D}{C}$$

$$V_1 = A \left(\frac{1}{C} I_1 + \frac{D}{C} I_2 \right) + B(-I_2)$$

$$= \frac{A}{C} I_1 + \frac{AD}{C} I_2 - B I_2$$

$$= \frac{A}{C} I_1 + \frac{(AD - BC)}{C} I_2$$


$$T_z = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \quad \Delta T = AD - BC$$

$$V_1 = \frac{A}{C} I_1 + \frac{\Delta T}{C} I_2 \quad : \quad \begin{array}{l} Z_{11} = A/C \\ Z_{12} = \frac{\Delta T}{C} \end{array}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} \rightarrow Z = \begin{bmatrix} A/C & \Delta T/C \\ 1/C & D/C \end{bmatrix}$$

Interconnection of 2 port networks.

"Cascade connection"

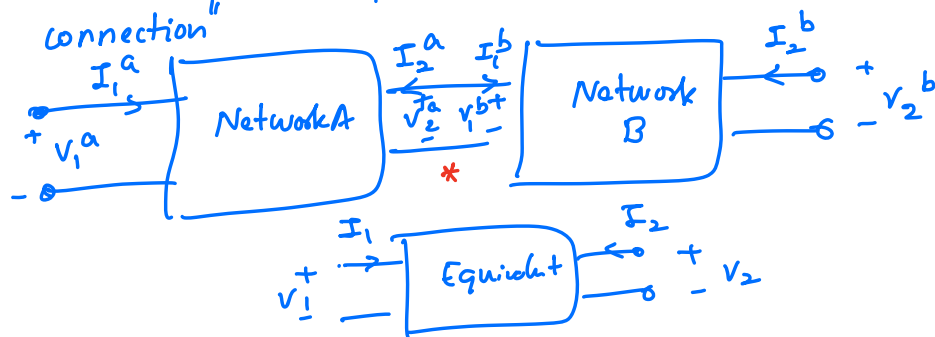

$$\begin{aligned}
 V_1 &= V_1^a & V_2 &= V_2^b \\
 I_1 &= I_1^a & I_2 &= I_2^b \\
 V_2^a &= V_1^b & I_2^a &= -I_1^b
 \end{aligned}$$

$$\begin{matrix} V_1 \\ I_1 \end{matrix} \begin{pmatrix} V_1^a \\ I_1^a \end{pmatrix} = \begin{pmatrix} A_a & B_a \\ C_a & D_a \end{pmatrix} \begin{pmatrix} V_2^a \\ -I_2^a \end{pmatrix} \begin{matrix} V_1^b \\ I_1^b \end{matrix}$$


$$\begin{pmatrix} V_1^b \\ I_1^b \end{pmatrix} \xleftarrow{\text{Network A}} \begin{pmatrix} A_b & B_b \\ C_b & D_b \end{pmatrix} \begin{pmatrix} V_2^b \\ -I_2^b \end{pmatrix} \begin{matrix} V_2 \\ -I_2 \end{matrix}$$

$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} A_a & B_a \\ C_a & D_a \end{pmatrix} \begin{pmatrix} A_b & B_b \\ C_b & D_b \end{pmatrix} \begin{pmatrix} V_2 \\ -I_2 \end{pmatrix}$$

$$[T] = [T_a] [T_b]$$

Inverse transmission
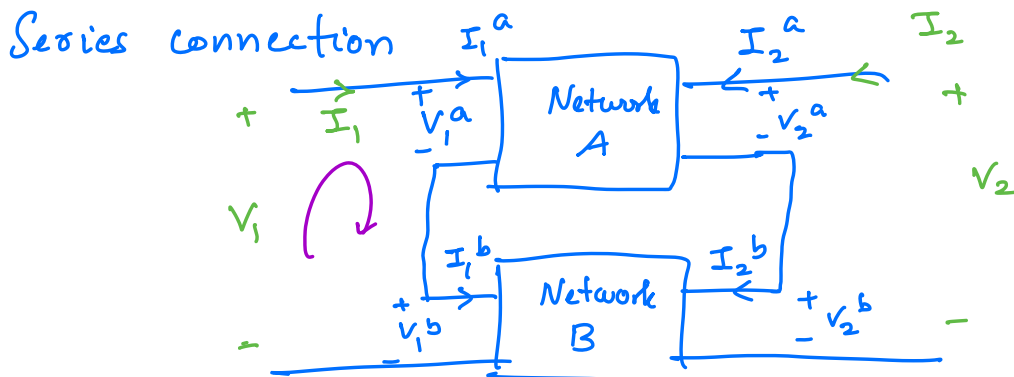
$$[T'] = [T'_b] [T'_a] \quad [\text{Exercise!}]$$



$$I_1 = I_1^a = I_1^b$$

$$I_2 = I_2^a = I_2^b$$

$$\begin{cases} V_1 = V_1^a + V_1^b \\ V_2 = V_2^a + V_2^b \end{cases}$$

$$\begin{pmatrix} V_1^a \\ V_2^a \end{pmatrix} = \begin{pmatrix} Z_{11}^a & Z_{12}^a \\ Z_{21}^a & Z_{22}^a \end{pmatrix} \begin{pmatrix} I_1^a \\ I_2^a \end{pmatrix}$$


$$\begin{pmatrix} V_1^b \\ V_2^b \end{pmatrix} = \begin{pmatrix} Z_{11}^b & Z_{12}^b \\ Z_{21}^b & Z_{22}^b \end{pmatrix} \begin{pmatrix} I_1^b \\ I_2^b \end{pmatrix}$$

$$\rightarrow \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} V_1^a \\ V_2^a \end{pmatrix} + \begin{pmatrix} V_1^b \\ V_2^b \end{pmatrix}$$

$$= \left(\begin{pmatrix} Z_{11}^a & Z_{12}^a \\ Z_{21}^a & Z_{22}^a \end{pmatrix} + \begin{pmatrix} Z_{11}^b & Z_{12}^b \\ Z_{21}^b & Z_{22}^b \end{pmatrix} \right) \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$

$$[Z] = [Z_a] + [Z_b]$$

Parallel Connection

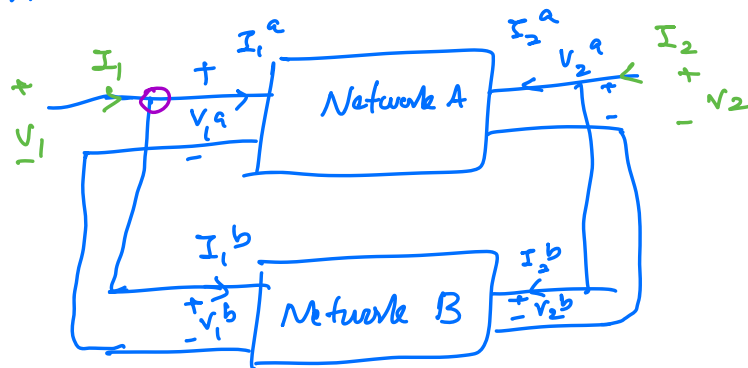

$$V_1 = V_1^a = V_1^b$$

$$V_2 = V_2^a = V_2^b$$

$$\begin{cases} I_1 = I_1^a + I_1^b \\ I_2 = I_2^a + I_2^b \end{cases}$$

$$\begin{pmatrix} I_1^a \\ I_2^a \end{pmatrix} = \begin{pmatrix} y_{11}^a & y_{12}^a \\ y_{21}^a & y_{22}^a \end{pmatrix} \begin{pmatrix} V_1^a \\ V_2^a \end{pmatrix} \quad \begin{matrix} V_1 \\ V_2 \end{matrix}$$

$$\begin{pmatrix} I_1^b \\ I_2^b \end{pmatrix} = \begin{pmatrix} y_{11}^b & y_{12}^b \\ y_{21}^b & y_{22}^b \end{pmatrix} \begin{pmatrix} V_1^b \\ V_2^b \end{pmatrix} \quad \begin{matrix} V_1 \\ V_2 \end{matrix}$$

$$\rightarrow \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} I_1^a \\ I_2^a \end{pmatrix} + \begin{pmatrix} I_1^b \\ I_2^b \end{pmatrix}$$

$$[Y] = [Y_a] + [Y_b]$$

Reciprocity



$$I_1' = I_2' \Rightarrow \text{Network is reciprocal}$$


Equivalent defn



$$V_1' = V_2' \\ \Rightarrow \text{N/w is reciprocal}$$



Symmetry

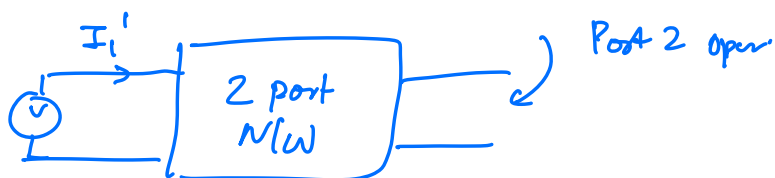

$$I_1' = I_2' \Rightarrow \text{Network is symmetrical}$$

Network being symmetrical (reciprocal

\Rightarrow Network parameters