

Announcements (i) Tutorial on Oct 13

(ii) Syllabus for Test 2

Part B: Lecture 1 - Lecture 6

[Basic understanding of Part A assumed]

Last class : Image parameters: Image impedance

Z_{im1} Z_{im2}

Image transfer constant

γ

Reciprocal N/w

$$Z_{im1} = \sqrt{\frac{AB}{CD}}$$

$$Z_{im2} = \sqrt{\frac{DB}{CA}}$$

$$e^{\gamma} = \sqrt{AD} + \sqrt{BC}$$

Reciprocal & Symmetrical N/w ($A = D$)

$$Z_{im1} = \sqrt{\frac{B}{C}}$$

$$Z_{im2} = \sqrt{\frac{B}{C}}$$


$$e^{\gamma} = \frac{A + \frac{B}{Z_0}}{1}$$

$$Z_{im1} = Z_{im2} = Z_0$$

$$\frac{V_1}{V_2} = \frac{I_1}{-I_2} = e^{\gamma}$$

Image parameters of a symmetrical T-network.

(Notation from SK 16.7.1)

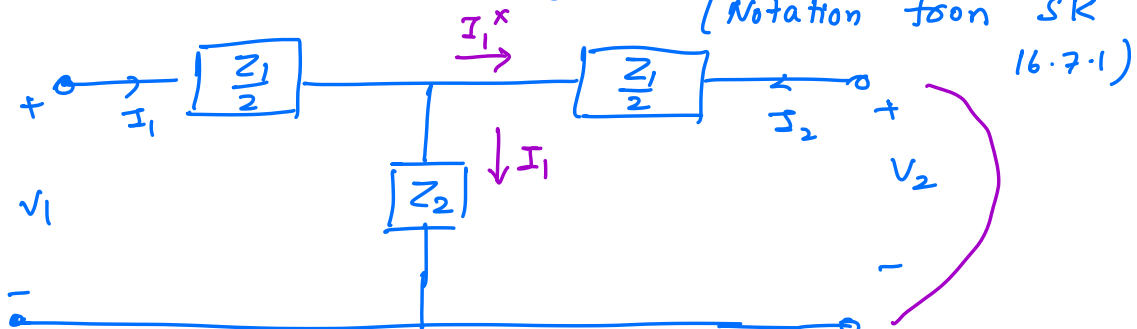

Transmission parameters

$$V_1 = A V_2 + B (-I_2)$$

$$I_1 = C V_2 + D (-I_2)$$

$$I_2 = 0 \quad A = \frac{V_1}{V_2} \quad V_2 = V_1 \cdot \frac{Z_2}{Z_2 + \frac{Z_1}{2}}$$

$$A = \frac{V_1}{V_2} = 1 + \frac{Z_1}{2Z_2}$$

$$C = \frac{I_1}{V_2}$$

$$V_2 = I_1 \cdot Z_2 \quad C = \frac{I_1}{V_2} = \frac{1}{Z_2}$$

$$V_2 = 0$$

$$B = \frac{V_1}{-I_2} = \frac{V_1}{I_1} \cdot \frac{I_1}{-I_2}$$

$$\frac{V_1}{I_1} = \frac{Z_1}{2} + Z_2 \parallel \frac{Z_1}{2} \quad - (1)$$

$$-I_2 = I_1 \cdot \frac{Z_2}{Z_2 + \frac{Z_1}{2}} \quad - (2)$$

$$B = \frac{V_1}{-I_2} = \left(\frac{Z_1}{2} + \frac{Z_1/2 \cdot Z_2}{Z_2 + \frac{Z_1}{2}} \right) \left(\frac{Z_2 + \frac{Z_1}{2}}{Z_2} \right)$$

$$= \frac{Z_1}{2} + \frac{Z_1}{2} \left(Z_2 + \frac{Z_1}{2} \right) \frac{1}{Z_2}$$

$$= \frac{Z_1}{2} + \frac{Z_1}{2} + \frac{Z_1^2}{4Z_2}$$

$$= Z_1 + \frac{Z_1^2}{4Z_2} = Z_1 \left(1 + \frac{Z_1}{4Z_2} \right)$$

$$D = A = 1 + \frac{Z_1}{2Z_2}$$

$$T = \begin{bmatrix} 1 + \frac{Z_1}{2Z_2} & Z_1 \left(1 + \frac{Z_1}{4Z_2}\right) \\ \frac{1}{Z_2} & 1 + \frac{Z_1}{2Z_2} \end{bmatrix}$$

$$Z_{im1} = Z_{im2} = Z_0 = \sqrt{B/C}$$

$$= \sqrt{\frac{Z_1 \left(1 + \frac{Z_1}{4Z_2}\right)}{\frac{1}{Z_2}}}$$

$$= \sqrt{Z_1 \left(Z_2 + \frac{Z_1}{4}\right)}$$


$$B = C \cdot Z_0^2$$

$$e^r = A + \frac{B}{Z_0}$$

$$= 1 + \frac{Z_1}{2Z_2} + C \cdot Z_0$$

$$= 1 + \frac{Z_1}{2Z_2} + \frac{Z_0}{Z_2} //$$

Symmetrical π -network. (Exercise)

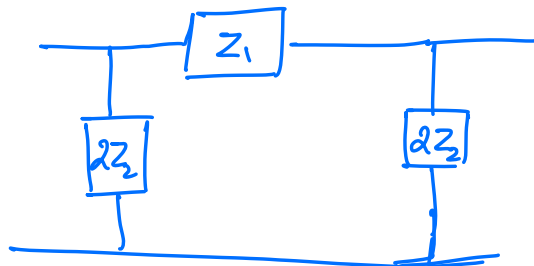

$$(Z_0)_\pi = \frac{Z_1 Z_2}{\sqrt{Z_1 \left(Z_2 + \frac{Z_1}{4}\right)}}$$

$$(Z_0)_T = \sqrt{Z_1 \left(Z_2 + \frac{Z_1}{4}\right)}$$

$$(Z_0)_\pi (Z_0)_T = Z_1 Z_2$$

$$(e^r)_\pi = (e^r)_T$$

Getting back to T-network.

$$e^r = 1 + \frac{Z_1}{2Z_2} + \frac{Z_0}{Z_2}$$

$$Z_2 e^r = Z_2 + \frac{Z_1}{2} + Z_0$$

$$\begin{aligned} Z_0 &= Z_2 (e^r - 1) - \frac{Z_1}{2} \\ Z_0 &= \sqrt{Z_1 \left(Z_2 + \frac{Z_1}{4} \right)} \\ Z_0^2 &= Z_1 Z_2 + Z_1^2/4 \end{aligned}$$

$$\left(Z_2 (e^r - 1) - \frac{Z_1}{2} \right)^2 = Z_1 Z_2 + Z_1^2/4$$

$$Z_2^2 (e^r - 1)^2 + \frac{Z_1^2}{4} - Z_1 Z_2 (e^r - 1) = \cancel{Z_1 Z_2} + \cancel{\frac{Z_1^2}{4}}$$

$$Z_2^2 (e^r - 1)^2 - Z_1 Z_2 e^r = 0$$

$$(e^r - 1)^2 = \frac{Z_1}{Z_2} \cdot e^r$$

$$e^{2r} - 2e^r + 1 = \frac{Z_1}{Z_2} \cdot e^r$$

$$e^r - 2 + e^{-r} = \frac{Z_1}{Z_2}$$

$$e^r + e^{-r} = 2 + \frac{Z_1}{Z_2}$$

$$\frac{e^r + e^{-r}}{2} = 1 + \frac{Z_1}{2Z_2}$$

$$\cosh(r) = 1 + \frac{Z_1}{2Z_2}$$

$$\parallel$$

$$1 + 2 \sinh^2\left(\frac{r}{2}\right)$$

$$\cancel{1} + 2 \sinh^2\left(\frac{r}{2}\right) = \cancel{1} + \frac{Z_1}{2Z_2}$$

$$\sinh\left(\frac{r}{2}\right) = \sqrt{\frac{Z_1}{4Z_2}} \parallel$$

Symmetrical
T. network

$$\frac{V_1}{V_2} = \frac{I_1}{-I_2} = e^r$$

$$r(j\omega) = \alpha(j\omega) + j \beta(j\omega)$$

$$V_2 = V_1 \cdot e^{-r}$$

$$= V_1 e^{-(\alpha(j\omega) + j \beta(j\omega))}$$

$$= V_1 \cdot e^{-\alpha(j\omega)} e^{-j \beta(j\omega)}$$

$$V_1 = V \angle 0 \quad \text{"Phasor notation"}$$


$$V_2 = V e^{-\alpha(j\omega)} \angle -\beta(j\omega)$$

↑
attenuation constant


↑
phase constant

At ω : $\alpha(j\omega) > 0 \Rightarrow$ Output gets attenuated

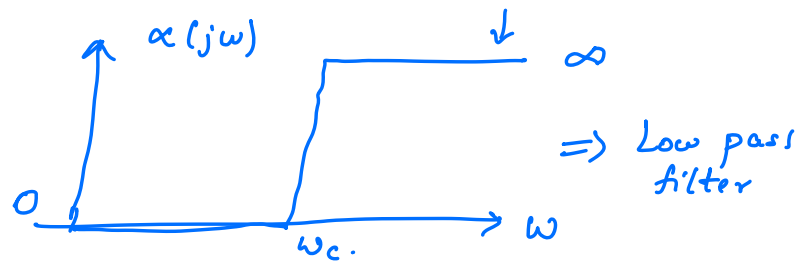$\alpha(j\omega) < 0 \Rightarrow$ Output gets amplified



Applications: Analog filters

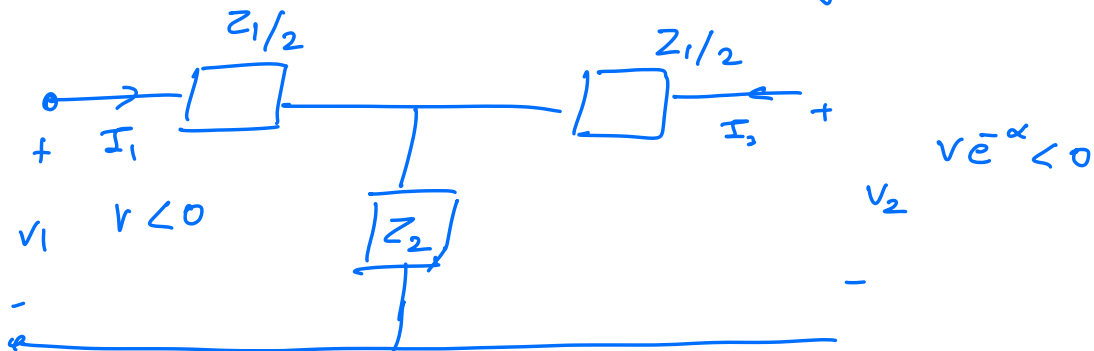

Case 1: Z_1 & Z_2 are of the same "type" reactance

↳ Z_1 & Z_2 capacitors

Z_1 & Z_2 inductors

$$\sinh\left(\frac{\gamma}{2}\right) = \sqrt{\frac{Z_1}{4Z_2}} = \sqrt{\frac{sL_1}{4sL_2}}$$

$$= \sqrt{\frac{L_1}{4L_2}} \quad (\text{real \& positive term})$$

$$\sinh\left(\frac{\gamma}{2}\right) = \sinh\left(\frac{\alpha + j\beta}{2}\right)$$

$$= \sinh\left(\frac{\alpha}{2}\right) \cos\left(\frac{\beta}{2}\right) + j \underbrace{\cosh\left(\frac{\alpha}{2}\right) \sin\left(\frac{\beta}{2}\right)}_0$$

= real & positive number

$\cosh(\cdot)$ always positive.
" "

$$\sin\left(\frac{\beta}{2}\right) = 0$$

$$\frac{\beta}{2} = 0, n\pi$$

$$\angle \beta(j\omega) = 0$$

$$\beta = 0, 2n\pi$$

$$\sinh\left(\frac{\alpha}{2}\right) \cos\left(\frac{\beta}{2}\right) = \sqrt{\frac{z_1}{4z_2}}$$

$$\frac{\alpha}{2} = \sinh^{-1}\left(\sqrt{z_1/4z_2}\right)$$

$$\alpha = 2 \sinh^{-1}\left(\sqrt{\frac{z_1}{4z_2}}\right) //$$