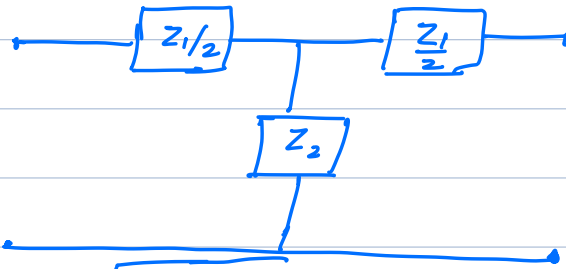


Announcements

1. No tutorial this week.

② Tutorial time to be confirmed (Some difficulties associated with Friday slot)
Wed 5-6pm → Fri 3-4pm?

Review



$$Z_0 = \sqrt{Z_1 Z_2 + Z_2^2/4}$$

$$r = \alpha + j\beta$$

$$Z_1 = j\omega L_1$$

$$Z_2 = j\omega L_2$$

Case A

$$\sinh\left(\frac{r}{2}\right) = \sqrt{\frac{Z_1}{4Z_2}}$$

Z_1 & Z_2 same reactance.

$$\alpha = 2 \sinh^{-1} \sqrt{\frac{Z_1}{4Z_2}}, \beta = 0$$

Case B:

Z_1 & Z_2 are of different reactance type.

$$Z_1(s) = sL$$

$$Z_1(j\omega) = j\omega L$$

$$Z_2(s) = \frac{1}{sC}$$

$$Z_2(j\omega) = \frac{1}{j\omega C}$$

$$\frac{Z_1}{4Z_2}(j\omega) = \frac{j\omega L}{4 \cdot \frac{1}{j\omega C}} = j^2 \frac{\omega^2 LC}{4} = \underline{\underline{\frac{-\omega^2 LC}{4}}}$$
$$\sqrt{\frac{Z_1}{4Z_2}} = j \left(\sqrt{\frac{\omega^2 LC}{4}} \right)$$

$$\sinh\left(\frac{\gamma}{2}\right) = \sqrt{\frac{Z_1}{4Z_2}}$$

$$\gamma = \alpha + j\beta$$

$$\sinh\left(\alpha + \frac{j\beta}{2}\right) = j \left| \sqrt{\frac{Z_1}{4Z_2}} \right|$$

$$\sinh\left(\frac{\alpha}{2}\right) \cosh\left(\frac{\beta}{2}\right) + j \cosh\left(\frac{\alpha}{2}\right) \underline{\sin\left(\frac{\beta}{2}\right)}$$

$$\text{Case (i)} \quad \sinh\left(\frac{\alpha}{2}\right) = 0 \quad \text{Case (ii)} = j \left| \sqrt{\frac{Z_1}{4Z_2}} \right|$$

$$\cosh\left(\frac{\beta}{2}\right) = 0 \quad \cosh\left(\frac{\beta}{2}\right) = 0$$


$$\text{Case (i)} \quad \sinh\left(\frac{\alpha}{2}\right) = 0$$

$$\Rightarrow \alpha = 0$$

$$\cosh\left(\frac{\alpha}{2}\right) \sin\left(\frac{\beta}{2}\right) = \left| \sqrt{\frac{Z_1}{4Z_2}} \right|$$

$$\underbrace{\cosh\left(\frac{\alpha}{2}\right)}_1$$

$$\sin\left(\frac{\beta}{2}\right) = \left| \sqrt{\frac{Z_1}{4Z_2}} \right|$$

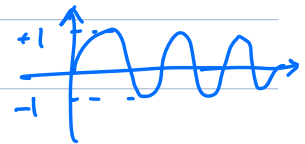

$$\beta = 2 \sin^{-1} \left(\left| \sqrt{\frac{Z_1}{4Z_2}} \right| \right)$$

$\alpha = 0$ (No attenuation)

$$\beta = 2 \sin^{-1} \left(\left| \sqrt{\frac{Z_1}{4Z_2}} \right| \right) \quad (\text{depends on freq of operation})$$

$$-1 \leq \frac{Z_1}{4Z_2} < 0$$

← +ve

$$\text{Case (ii)} \quad \cosh\left(\frac{\beta}{2}\right) = 0$$

$$\frac{\beta}{2} = (2n-1) \pi/2 \quad \beta = (2n-1) \pi$$

$$\beta = \pi, 3\pi, 5\pi \dots$$

$$\beta = \pi$$

$$\cosh\left(\frac{\alpha}{2}\right) \underbrace{\sin\left(\frac{\beta}{2}\right)}_1 = \left| \sqrt{\frac{Z_1}{4Z_2}} \right|$$

$$\cosh(x) = \frac{e^x + e^{-x}}{2}$$

$$\cosh\left(\frac{\alpha}{2}\right) = \left| \sqrt{\frac{Z_1}{4Z_2}} \right|$$

$$\alpha = 2 \cosh^{-1} \left(\left| \sqrt{\frac{Z_1}{4Z_2}} \right| \right)$$

$$\frac{Z_1}{4Z_2} \leq -1$$

$$\frac{Z_1}{4Z_2} \leq -1$$

$$\alpha = 2 \cosh^{-1} \left(\sqrt{\frac{Z_1}{4Z_2}} \right) \text{ (depends on frequency)}$$

$$\beta = \pi$$

$$-1 \leq \frac{Z_1}{4Z_2} < 0$$

$$\alpha = 0$$


$$\beta = 2 \sin^{-1} \left(\sqrt{\frac{Z_1}{4Z_2}} \right)$$

$$\frac{Z_1}{4Z_2} \leq -1$$

$$\alpha = 2 \cosh^{-1} \left(\sqrt{\frac{Z_1}{4Z_2}} \right)$$

$$\beta = \pi$$

LPF

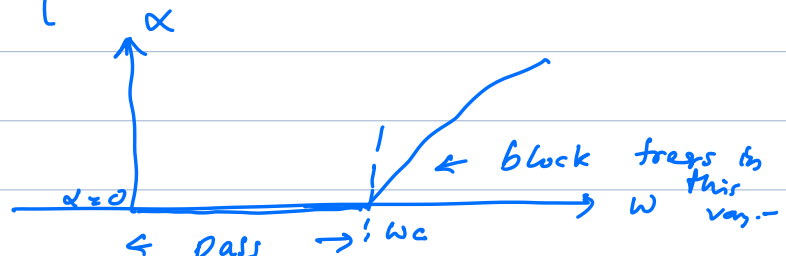

At $\omega = \omega_c$: $\frac{Z_1(j\omega_c)}{4 Z_2(j\omega_c)} = -1$

frequency
in this row

$$Z_1(j\omega_c) + 4 Z_2(j\omega_c) = 0$$

Network Synthesis \rightarrow Simple L & C

1) Constant k

$$Z_1(j\omega_c) = j\omega_c L$$

2) m - assumptions

$$Z_2(j\omega_c) = \frac{1}{j\omega_c C}$$

T-circuit

