

Announcements: Problem Set posted

Cut-set  $Q_a$   $Q_f$


$$Q_f = \begin{bmatrix} I_{n-1} & Q_{fc} \end{bmatrix}$$

← tree →      ← links →


Properties [skipping the proofs]

1. v-shift property

independent voltage source.

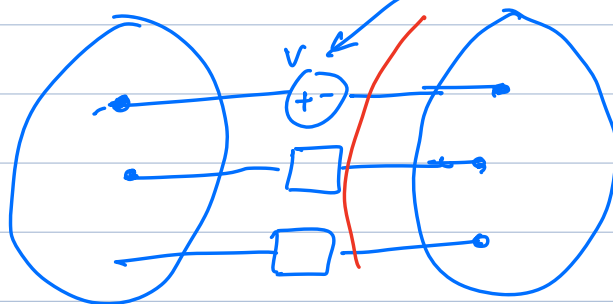


$\Leftrightarrow$

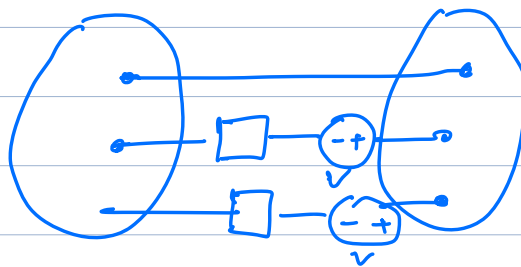


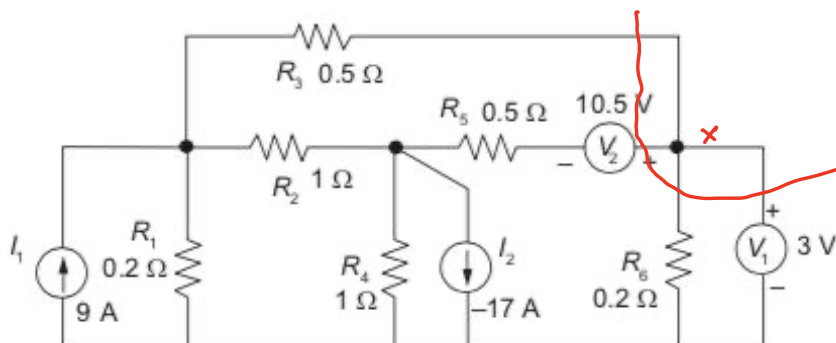Example:

Nodal analysis (using A matrix) (current sources)


Voltage sources  $\xRightarrow{\text{Source Txn}}$  Current Sources



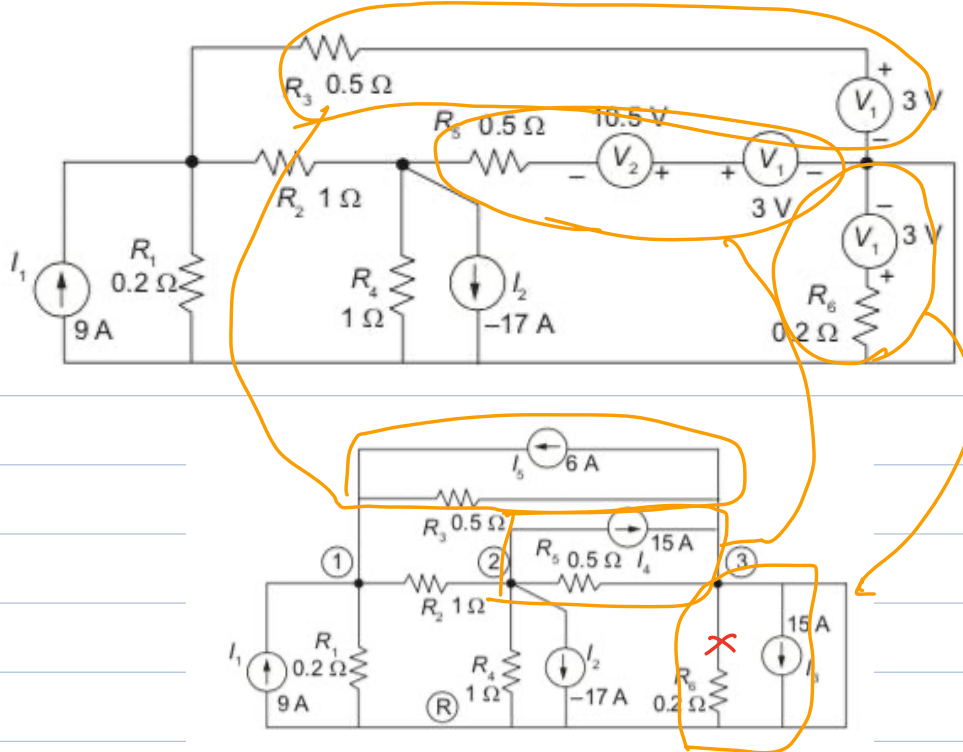

Analyze this ckt using nodal analysis!



2.  $i$ -shift

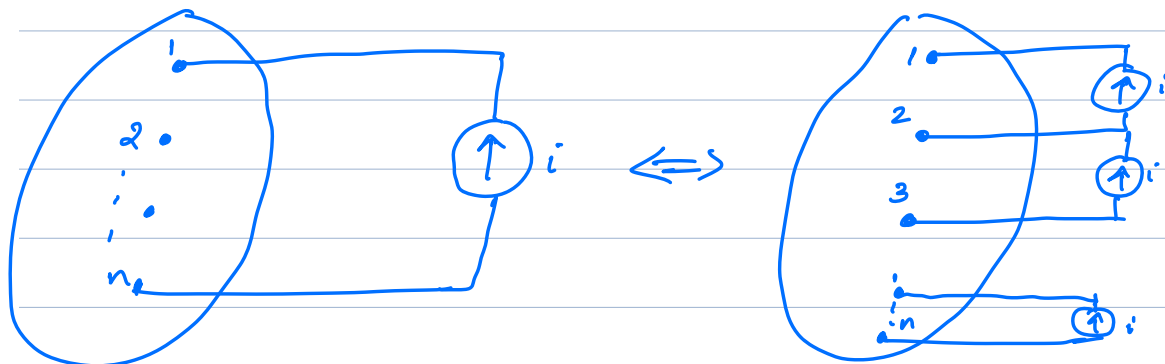


Nodes 1 to  $n$  form a loop with the current source  $i$ .

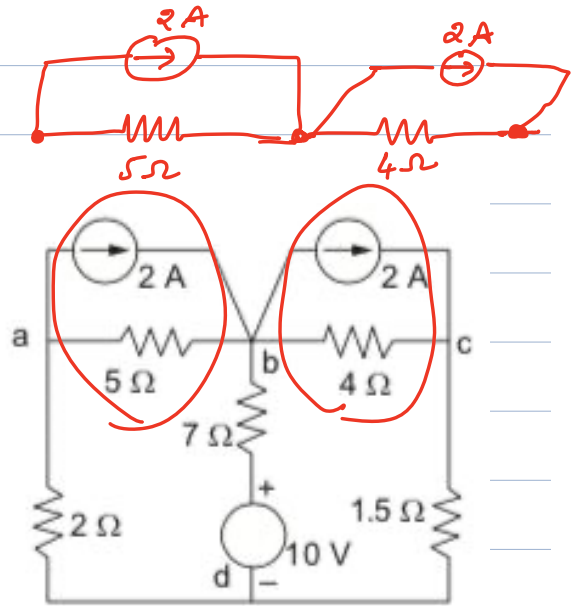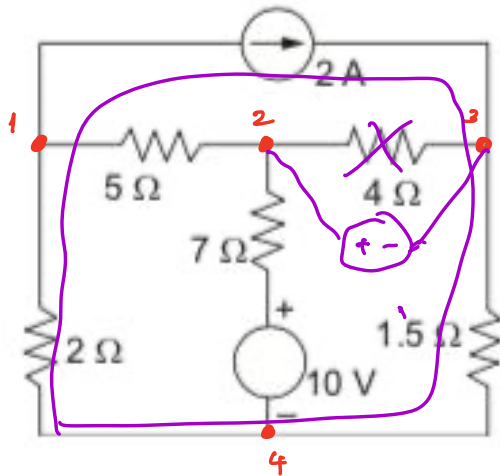Example:

Mesh analysis using B matrix + Voltage sources  
Current sources  $\Rightarrow$  Voltage Sources



Do analysis using B matrix!

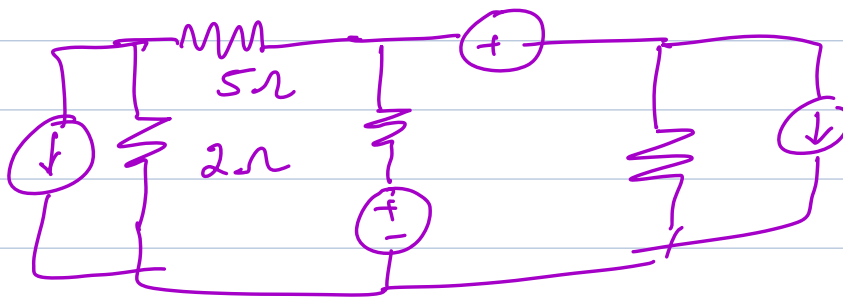

3. Orthogonal relation b/w  $Q_f$  & B matrix

Fix  
a tree

$$Q_f B_f^T = 0$$

$$\dim(Q_f) = (n-1) \times b$$

$$\dim(B_f) = (b - (n-1)) \times b$$

tree , links

$$\begin{cases} Q_f = [ I_{n-1} & Q_{fe} ] \\ B_f = [ B_{ft} & I ] \end{cases}$$

$$[ I \quad Q_{fe} ] \begin{bmatrix} B_{ft}^T \\ I \end{bmatrix} = 0$$

$$B_{ft}^T + Q_{fe} = 0$$

$$Q_{fe} = -B_{ft}^T$$

KCL equations (in terms of  $Q$ )

$$i_t = B_{ft}^T i_e$$

$$i_t = -Q_{fe} i_e$$

$$i = \begin{bmatrix} i_t \\ i_e \end{bmatrix} = \begin{bmatrix} -Q_{fe} i_e \\ i_e \end{bmatrix}$$

$$= \begin{bmatrix} -Q_{fe} \\ I \end{bmatrix} i_e$$

$$Q_f i = [ I \quad Q_{fe} ] i$$

$$= [ I \quad Q_{fe} ] \begin{bmatrix} -Q_{fe} \\ I \end{bmatrix} i_e$$

$$Q_f i = 0$$

KVL equations (in terms of  $Q$ )

$$B_f \cdot v = 0 \quad (\text{KVL eqn in terms of } B)$$

$$[ B_{ft} \quad I ] \begin{bmatrix} v_t \\ v_e \end{bmatrix} = 0$$

$$B_{ft} v_t + v_e = 0$$

$$v_e = -B_{ft} \cdot v_t = Q_{fe}^T v_t$$

$$v = \begin{bmatrix} v_t \\ v_e \end{bmatrix} = \begin{bmatrix} v_t \\ Q_{fe}^T v_t \end{bmatrix}$$

$$= \begin{bmatrix} I \\ Q_{fe}^T \end{bmatrix} v_t$$

$$v = Q_f^T v_t$$

Analysis using  $Q$  matrix  $\Rightarrow$  Do next class