

Last class: 2 port network parameters

- 2- parameters

- Y- parameters

Hybrid parameters (h- parameters)

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned} \quad \left| \quad \begin{pmatrix} V_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{pmatrix} \begin{pmatrix} I_1 \\ V_2 \end{pmatrix} \right.$$


$$h_{11} = \frac{V_1}{I_1} \bigg|_{V_2=0} \quad \begin{array}{l} \text{input impedance w/} \\ \text{output shorted} \end{array}$$

$$h_{21} = \frac{I_2}{I_1} \bigg|_{V_2=0} \quad \begin{array}{l} \text{forward current gain} \\ \text{output shorted} \end{array}$$


$$h_{12} = \frac{V_1}{V_2} \bigg|_{I_1=0} \quad \begin{array}{l} \text{reverse voltage gain} \\ \text{input open} \end{array}$$

$$h_{22} = \frac{I_2}{V_2} \bigg|_{I_1=0} \quad \begin{array}{l} \text{output admittance} \\ \text{input open} \end{array}$$

Equivalent circuit

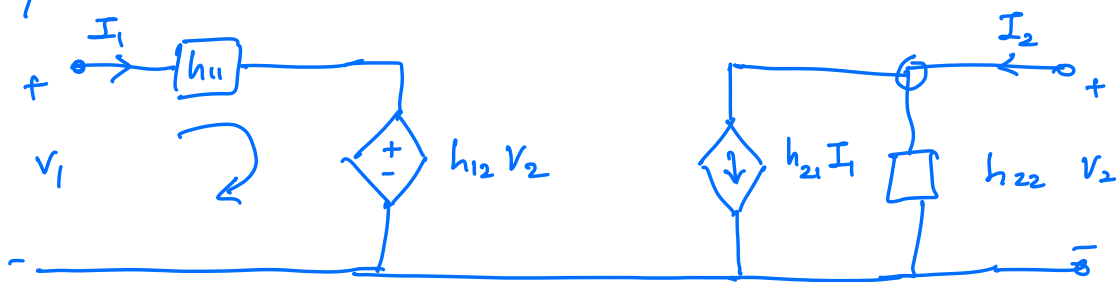

Example 16.15 in SK

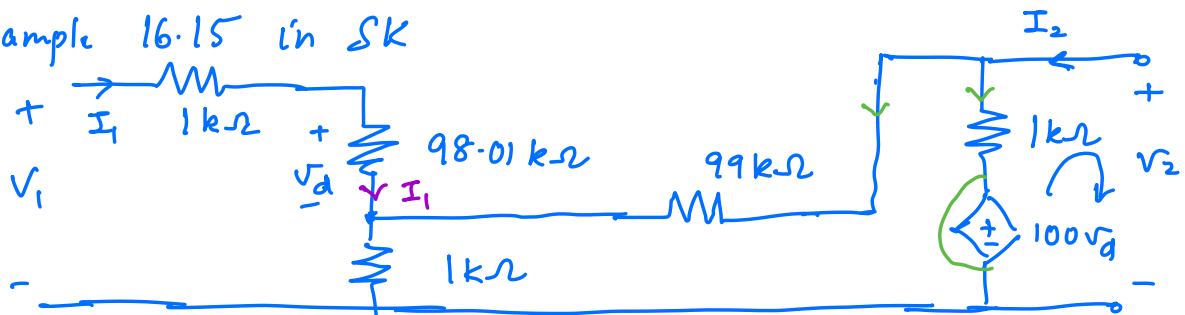

$$h_{11} \text{ f } h_{21} \quad V_2 = 0$$

$$\boxed{I_1 = 0 \quad V_d = 0}$$

$$h_{11} = \frac{V_1}{I_1} \quad V_1 = I_1 (1 \text{ k}\Omega + 98.01 \text{ k}\Omega + 1 \text{ k}\Omega \parallel 99 \text{ k}\Omega)$$

$$= I_1 \cdot 100 \text{ k}\Omega$$

$$h_{11} = \frac{V_1}{I_1} = 100 \text{ k}\Omega //$$

$$100 V_d + 1 \text{ k}\Omega \times I_x = 0$$

$$h_{21} = I_2 / I_1 \mid V_2 = 0$$

$$I_2 = I_x + I_y$$

$$I_x = - \frac{100 V_d}{1 \text{ k}\Omega}$$

$$-I_y = I_1 \times \frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 99 \text{ k}\Omega} = \frac{I_1}{100}$$

$$V_d = I_1 \times 98.01 \text{ k}\Omega$$

$$I_x = - \frac{100}{1 \text{ k}\Omega} \times 98.01 \text{ k}\Omega \times I_1$$


$$= -9801 I_1$$

$$I_2 = I_x + I_y = -9801 I_1 - \frac{I_1}{100}$$

$$\frac{I_2}{I_1} \approx -9801 //$$

$$h_{12} \text{ f } h_{22} \quad I_1 = 0$$

$$h_{22} = I_2 / V_2 \mid I_1 = 0$$

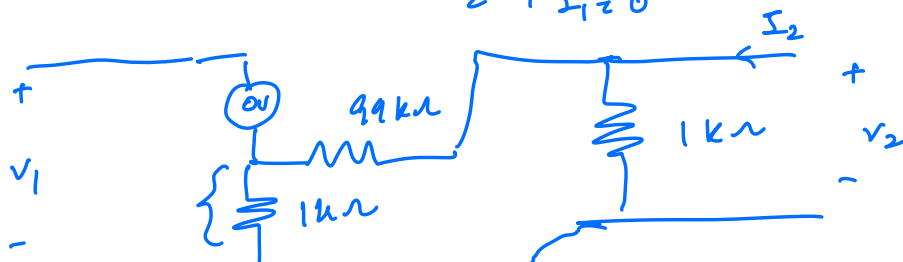

$$\frac{I_2}{V_2} = \frac{V_2}{V_2} = \frac{1}{1k\Omega \parallel 100k\Omega} \approx \frac{1}{1k\Omega}$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0}$$

$$V_1 = V_2 \cdot \frac{1k\Omega}{1k\Omega + 99k\Omega} = V_2 \cdot \frac{1}{100}$$

$$\frac{V_1}{V_2} = \frac{1}{100} //$$

Inverse hybrid parameters

$$\begin{cases} I_1 = g_{11} V_1 + g_{12} I_2 \\ V_2 = g_{21} V_1 + g_{22} I_2 \end{cases} \quad \left| \quad \begin{pmatrix} I_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{pmatrix} \begin{pmatrix} V_1 \\ I_2 \end{pmatrix} \right.$$

$$\begin{pmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{pmatrix} = \begin{pmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{pmatrix}^{-1}$$


$$g_{11} = \frac{I_1}{V_1} \Big|_{I_2=0} \quad \text{input admittance with o/p open}$$

$$g_{21} = \frac{V_2}{V_1} \Big|_{I_2=0} \quad \text{forward voltage gain with o/p open}$$

$$g_{12} = \frac{I_1}{I_2} \Big|_{V_1=0} \quad \text{reverse current gain with i/p short}$$

$$g_{22} = \frac{V_2}{I_2} \Big|_{V_1=0} \quad \text{output impedance with i/p short}$$

Equivalent ckt

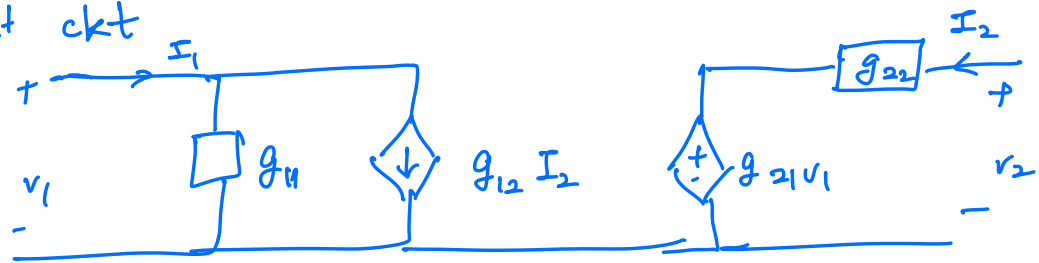

Transmission Parameters (ABCD parameters)


$$V_1 = A V_2 + B (-I_2)$$

$$I_1 = C V_2 + D (-I_2)$$

$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_2 \\ -I_2 \end{pmatrix}$$

← Port 1 →

← Port 2 →

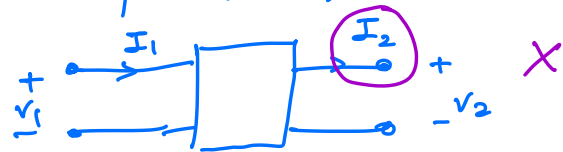

$$A = \left. \frac{V_1}{V_2} \right|_{I_2 = 0} \quad : \text{Reverse voltage gain}$$


$$C = \left. \frac{I_1}{V_2} \right|_{I_2 = 0} \quad : \text{open ckt transfer admittance}$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2 = 0} \quad : \text{Short ckt transfer impedance}$$

$$D = \left. \frac{I_1}{-I_2} \right|_{V_2 = 0} \quad : \text{Reverse current gain}$$

Example 16.2.1 in SK

[Find the steady state ABCD parameters]

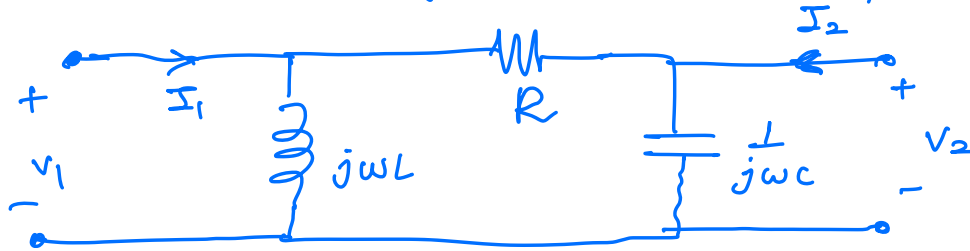

A FC $I_2 = 0$

$$A = \frac{V_1}{V_2}$$

$$V_2 = V_1 \frac{Y_{j\omega C}}{R + Y_{j\omega C}}$$


$$= \frac{V_1}{1 + j\omega RC}$$

$$A = \frac{V_1}{V_2} = \underline{\underline{1 + j\omega RC}}$$

$$C = \frac{I_1}{V_2} \Big|_{I_2 = 0}$$

$$I_1 = ? \quad V_1$$
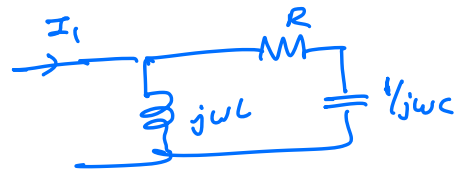
$$I_1 = \frac{V_1}{j\omega L \parallel (R + \frac{1}{j\omega C})}$$



$$= \frac{V_1}{j\omega L \parallel (R + \frac{1}{j\omega C})}$$

$$= \frac{V_1}{j\omega L (R + \frac{1}{j\omega C})}$$

$$= \frac{V_1}{\frac{j\omega L (1 + j\omega RC)}{1 + j\omega C (R + j\omega L)}}$$

$$= V_1 \cdot \frac{[1 + j\omega C (R + j\omega L)]}{j\omega L (1 + j\omega RC)}$$

✓

$$= (1 + j\omega R C) V_2 \frac{[1 + j\omega C (R + j\omega L)]}{j\omega C (1 + j\omega R C)}$$

$$\frac{I_1}{V_2} = \frac{1 + j\omega C (R + j\omega L)}{j\omega C}$$

Exercise : Find B & D ?

$$B = R$$

$$D = 1 + R/j\omega L$$