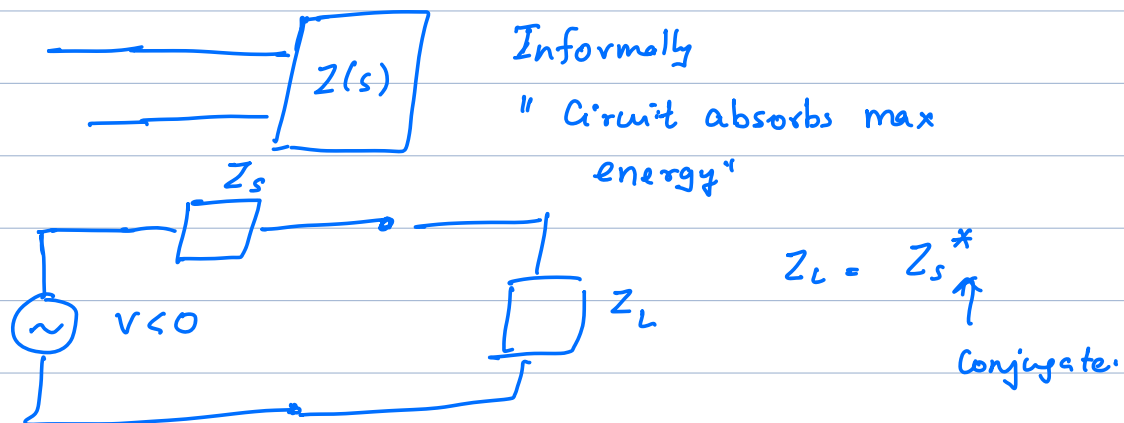


Announcement: Quiz 2 on Nov 20, 4pm  
(4pm - 5:30pm) + Sec

## Resonance



Resonant freq of a ckt is defined as the freq where the ckt behaves purely resistive.

"Q-factor"

Review: Power & Energy in Sinusoidal steady state

$$\begin{aligned}
 & I_m \angle \phi \rightarrow [Z(s)] \rightarrow V_m \angle \theta \\
 & I_m e^{j(\omega t + \phi)} \quad Z(j\omega) = |Z(j\omega)| \angle \angle Z(j\omega) \\
 & V_m = I_m |Z(j\omega)| \\
 & \theta = \phi + \angle Z(j\omega)
 \end{aligned}$$

$$v(t) = V_m \cos(\omega t + \theta)$$

$$i(t) = I_m \cos(\omega t + \phi)$$

Instantaneous power  $p(t) = v(t) i(t)$

$$p(t) = V_m I_m \cos(\omega t + \theta) \cos(\omega t + \phi)$$

$$= \frac{V_m I_m}{2} \left[ \underbrace{\cos(\theta - \phi)}_{\text{constant}} + \underbrace{\cos(2\omega t + \theta + \phi)}_{\text{time-varying}} \right]$$

$$\text{Average power } P = \frac{1}{T} \int_0^T p(t) \cdot dt$$

$$= \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \left[ \cos(\theta - \phi) + \cos(2\omega t + \theta + \phi) \right] dt$$

$$= \frac{V_m \cdot I_m}{2} \cdot \cos(\theta - \phi)$$


$I_m \angle \phi$        $V = R I_m \angle \phi$

Special Cases : 1. Resistor



$$\text{Avg Power (R)} = \frac{I_m^2 R}{2}$$

2. Capacitor / Inductor

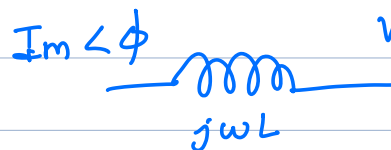

$$V = \omega L \cdot I_m \angle \phi + 90^\circ$$

$$\text{Avg. Power (L)} = 0$$

$$\text{Avg. Power (C)} = 0$$

Energy "stored" by a capacitor.

$$E(t) = \int_0^t p(t) dt$$

$$= \int_0^t v(t) \cdot i(t) dt$$

$$i(t) = C \cdot \frac{dv(t)}{dt}$$

$$\begin{aligned}
 & \overline{\frac{d}{dt}} \\
 &= \int_0^t C \cdot v(t) \cdot \frac{dv(t)}{dt} \cdot dt \\
 &= \frac{1}{2} C \cdot [v^2(t) - v^2(0)]
 \end{aligned}$$


Ass: Initial voltage of capacitor = 0  $\rightarrow v(0) = 0$

$$E(t) = \frac{1}{2} \cdot C \cdot v^2(t)$$

Inductor case:  $E(t) = \frac{1}{2} \cdot L \cdot i^2(t)$

$$\begin{aligned}
 \text{Q-factor} &= \frac{2\pi \cdot \text{Max energy stored per cycle}}{\text{Energy dissipated per cycle}} \\
 &[\text{Sinusoidal Steady state}]
 \end{aligned}$$

Example: (Leaky Capacitor)

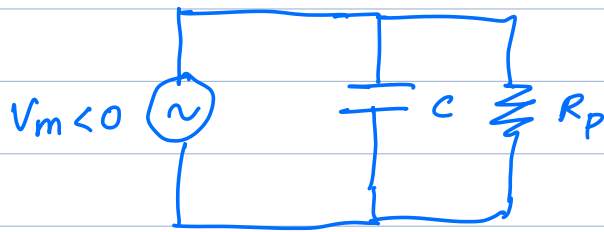

Max energy stored per cycle:

$$E(t) = \frac{1}{2} \cdot C \cdot v^2(t)$$

$$E_{max} = \frac{1}{2} C \cdot v_m^2$$

$$\text{Power dissipated by } R_p = \frac{1}{2} \cdot \frac{v_m^2}{R_p}$$

$$\text{Energy dissipated by } R_p = \frac{1}{2} \cdot \frac{V_m^2}{R_p} \cdot T$$


$$= \frac{1}{2} \cdot \frac{V_m^2}{R_p} \cdot \frac{1}{f}$$

Q-factor (Leaky Cap)


$$= \frac{2\pi \cdot \cancel{\frac{1}{2}} \cdot C \cdot \cancel{V_m^2}}{\frac{1}{2} \cdot \frac{V_m^2}{R_p} \cdot \frac{1}{f}}$$

$$= \omega \cdot R_p \cdot C //$$

Exercise:

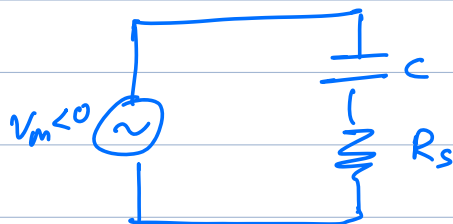


Inductor Case: Lossy Inductor:

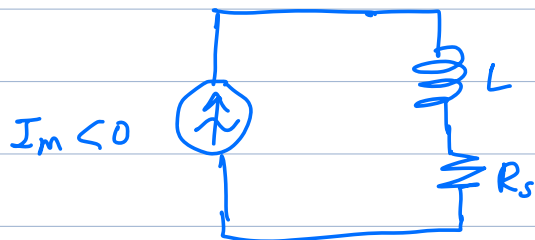

Q-factor (Lossy Inductor)

$$= \omega \frac{L}{R_s} //$$

Series RLC circuit


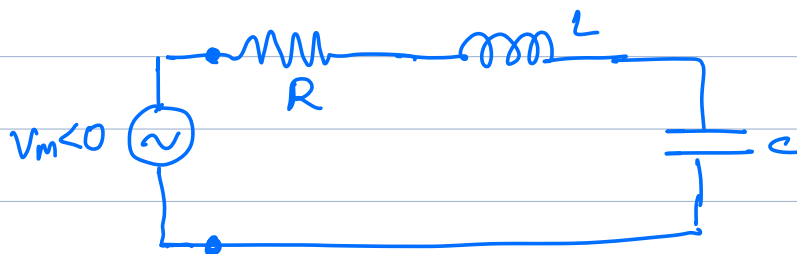


$$Z(j\omega) = R + j\omega L + \frac{1}{j\omega C}$$

$$= R + j\omega L - \frac{j}{\omega C}$$


Resonant frequency  $\omega_0 L = \frac{1}{\omega_0 C} \Rightarrow Z$  is purely resistive.
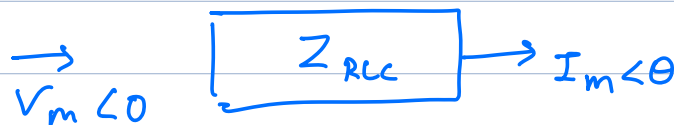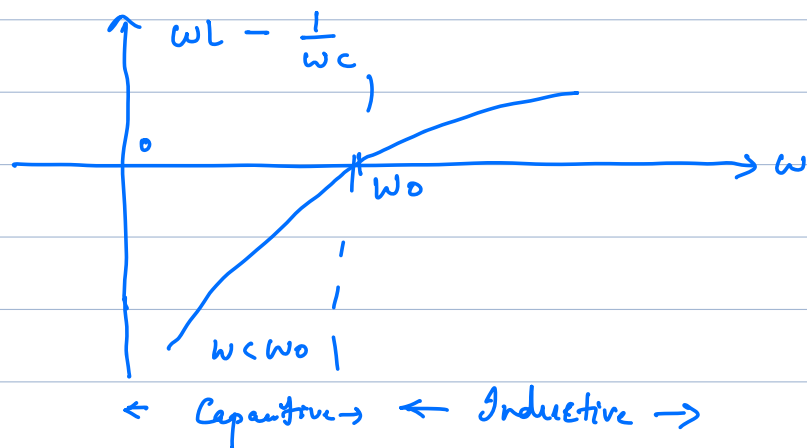
$$\omega_0^2 = \frac{1}{LC} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$



$$I_m = \frac{V_m}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$
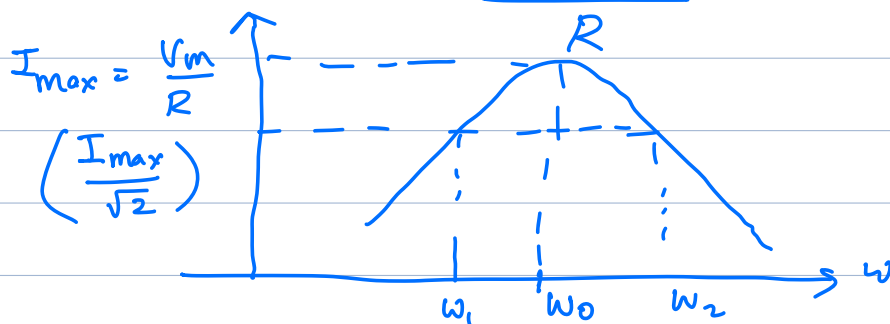
$$\theta = \tan^{-1} \left( \omega L - \frac{1}{\omega C} \right)$$



$\omega_1, \omega_2$  : Half power frequency (3dB)