
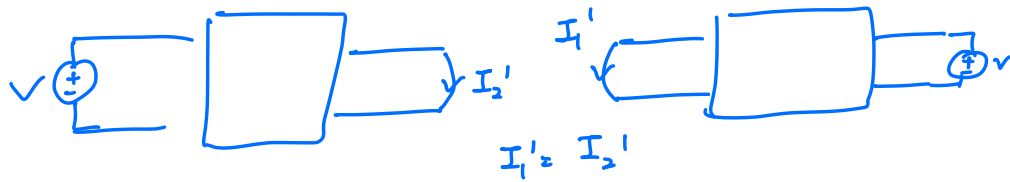


Reciprocity

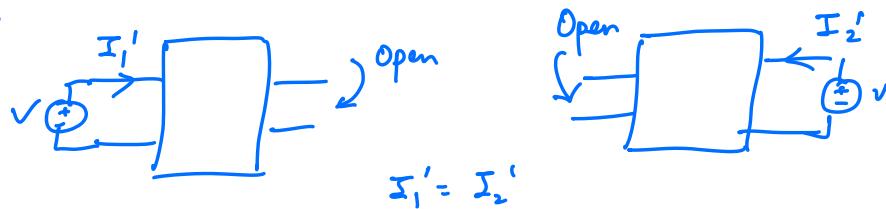

Symmetry



Reciprocity of Z-parameters

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$V_2 = 0$$

$$0 = Z_{21} I_1 + Z_{22} I_2$$

$$I_1 = -\frac{Z_{22}}{Z_{21}} I_2$$

$$V = Z_{11} - \frac{Z_{22}}{Z_{21}} I_2 + Z_{12} I_2$$

$$V = -\frac{\Delta Z}{Z_{21}} I_2 \Rightarrow I_2' = V \cdot \frac{Z_{21}}{\Delta Z}$$

$$0 = Z_{11} I_1 + Z_{12} I_2$$

$$I_2 = -\frac{Z_{11}}{Z_{12}} I_1$$

$$V = Z_{21} I_1 + Z_{22} - \frac{Z_{11}}{Z_{12}} I_1 = -\frac{\Delta Z}{Z_{12}} I_1$$



$$I_1 = -V \frac{Z_{12}}{\Delta Z} \Rightarrow I_1' = V \cdot \frac{Z_{12}}{\Delta Z}$$

ΔZ ΔZ

$$I_1' = I_2' \Rightarrow Z_{12} = Z_{21}$$

"Reciprocity in Z-parameter"

Symmetry

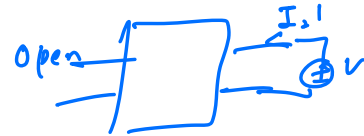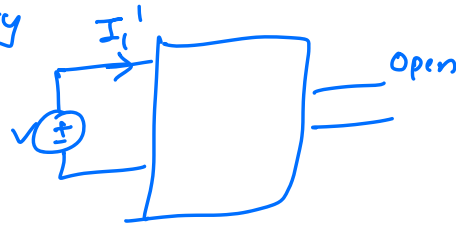

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$I_1' = I_1 = \frac{V}{Z_{11}}$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$


$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$I_2' = I_2 = V / Z_{22}$$

$$Z_{11} = Z_{22}$$

"Symmetry in Z-parameter"

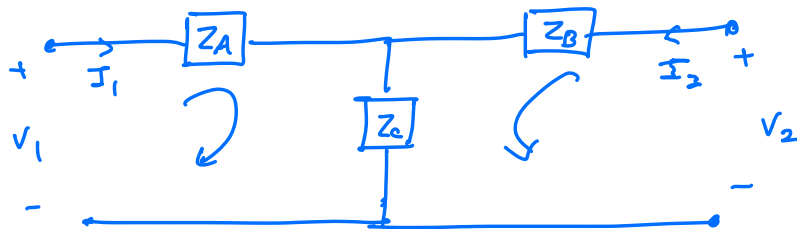T equivalent of a reciprocal 2 port network.



$$V_1 = I_1 Z_A + (I_1 + I_2) Z_c = (Z_A + Z_c) I_1 + Z_c I_2$$

$$V_2 = I_2 Z_B + (I_1 + I_2) Z_c = Z_c I_1 + (Z_B + Z_c) I_2$$


$$* Z = \begin{pmatrix} Z_A + Z_c & Z_c \\ Z_c & Z_B + Z_c \end{pmatrix} \quad Z_{21} = Z_{12}$$

Y-parameters : Exercise

Reciprocity : $Y_{12} = Y_{21}$

Symmetry : $Y_{11} = Y_{22}$

π -equivalent of a reciprocal 2-port N/w

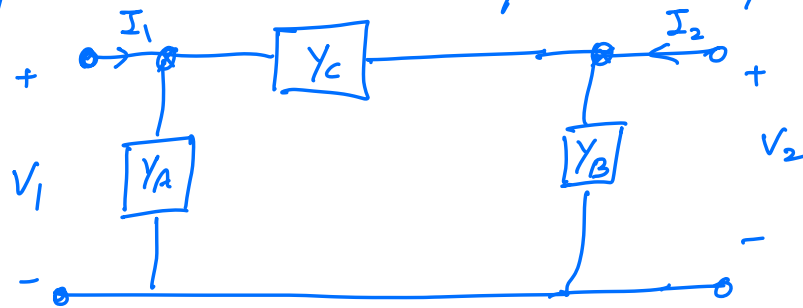



$$\begin{aligned} I_1 &= V_1 \cdot Y_A + (V_1 - V_2) Y_C \\ &= (Y_A + Y_C) V_1 + (-Y_C) V_2 \end{aligned}$$

$$\begin{aligned} I_2 &= V_2 \cdot Y_B + Y_C \cdot (V_2 - V_1) \\ &= (-Y_C) V_1 + (Y_B + Y_C) V_2 \end{aligned}$$


$$* Y = \begin{pmatrix} Y_A + Y_C & -Y_C \\ -Y_C & Y_B + Y_C \end{pmatrix} \quad Y_{12} = Y_{21}$$

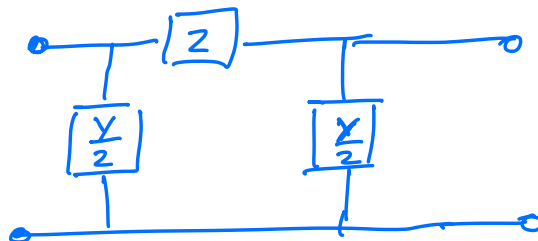T & π equivalent for reciprocal & symmetric
(Exercise)



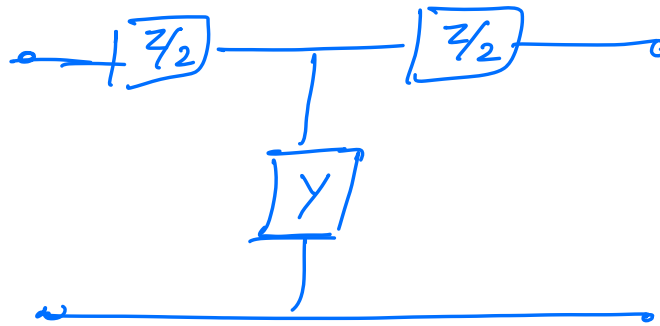

Transmission Parameters

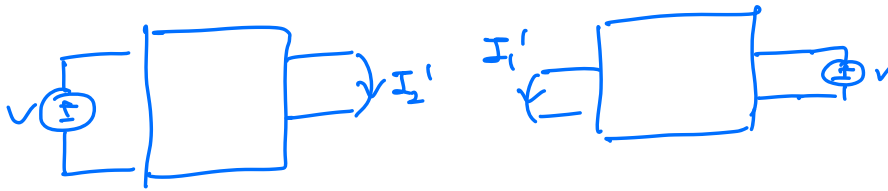

$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_2 \\ -I_2 \end{pmatrix}$$

$$V_2 = 0$$

$$V = V_1 = B(-I_2)$$

$$I_2 = -\frac{V}{B}$$

$$I_1' = \frac{V}{B}$$

$$\frac{V}{B} = \frac{\Delta T \cdot V}{B}$$

$$\Delta T = 1$$

$$\det \begin{pmatrix} A & B \\ C & D \end{pmatrix} = 1$$

Symmetry: $A = D$

$$V_1 = 0$$

$$0 = A \cdot V - B I_2$$

$$I_2 = \frac{A \cdot V}{B}$$

$$I_1 = C \cdot V - D I_2$$

$$= C \cdot V - D \frac{A \cdot V}{B}$$

$$= -\frac{\Delta T \cdot V}{B}$$

$$I_1' = \frac{\Delta T \cdot V}{B}$$

Inverse Transmission Parameters

$$R: \det \begin{pmatrix} A' & B' \\ C' & D' \end{pmatrix} = 1$$


$$S: A' = D'$$

Hybrid Parameters

Reciprocity: $h_{12} = -h_{21}$

Symmetry: $\Delta H = 1$

Next parametrization: Image Impedance

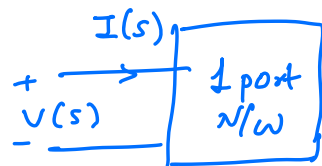

Input Impedance/
Impedance

$$Z(s) = \frac{V(s)}{I(s)}$$



Driving point impedance at port p

$$= \frac{V_p(s)}{I_p(s)}$$



$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$V_2 = -I_2 \cdot Z_L$$

$$-I_2 \cdot Z_L = Z_{21} I_1 + Z_{22} I_2$$

$$I_2 = -\frac{Z_{21} I_1}{Z_L + Z_{22}}$$

$$V_1 = Z_{11} I_1 - \frac{Z_{12} Z_{21} I_1}{Z_L + Z_{22}}$$

$$\frac{V_1}{I_1} = Z_{11} - \frac{Z_{12} Z_{21}}{Z_L + Z_{22}}$$

$$\begin{aligned} Z_{10} &= \text{Driving point impedance} \\ &\quad \uparrow \text{Open} \quad \text{on } Z_L \rightarrow \infty \\ &= Z_{11} \end{aligned}$$

$$\begin{aligned} Z_L = 0 \quad Z_{1S} &= Z_{11} - \frac{Z_{12} Z_{21}}{Z_{22}} \\ &\quad \uparrow \text{Short} \\ &= \frac{\Delta Z}{Z_{22}} \\ &= \frac{1}{Y_{11}} \end{aligned}$$

Exercise



$$\frac{V_2}{I_2} = Z_{22} - \frac{Z_{12} Z_{21}}{Z_{11} + Z_L}$$

$$\begin{aligned} Z_{20} &= Z_{22} \\ &\quad \uparrow \text{Port 1 is open} \end{aligned}$$

$$\begin{aligned} Z_{2S} &= Z_{22} - \frac{Z_{12} Z_{21}}{Z_{11}} \\ (Z_L = 0) & \\ &= \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{11}} \\ &= \Delta Z / Z_{11} = \frac{1}{Y_{22}} \end{aligned}$$

$$\begin{array}{rclcl}
 Z_{10} & = & Z_{11} & = & \frac{A}{C} \\
 Z_{15} & = & Y_{11} & = & B/D \\
 Z_{20} & = & Z_{22} & = & D/C \\
 Z_{25} & = & Y_{22} & = & B/A
 \end{array}
 \left. \vphantom{\begin{array}{rclcl} Z_{10} & = & Z_{11} & = & \frac{A}{C} \\ Z_{15} & = & Y_{11} & = & B/D \\ Z_{20} & = & Z_{22} & = & D/C \\ Z_{25} & = & Y_{22} & = & B/A \end{array}} \right\} \text{Use the lookup}$$