

Last class : Basic terminology of graphs : Path, Loop
Incidence matrix, Tree

Tree


$$A = [A_t : A_l]$$

$$\dim(A_t) = (n-1) \times (n-1)$$

$$\dim(A_l) = (n-1) \times (b - (n-1))$$

Property: $\text{Rank}(A_t) = n-1$ [Invertible]

KVL & KCL

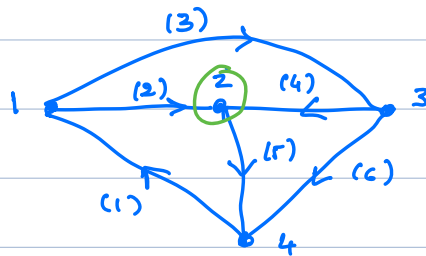

$$A = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 3 \end{matrix} & \begin{bmatrix} -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 0 & -1 & 1 & 0 \\ 0 & 0 & -1 & -1 & 0 & 1 \end{bmatrix} \end{matrix}$$

$\begin{matrix} (1) & (2) & (3) & (4) & (5) & (6) \\ \rightarrow i_{(1)} & i_{(2)} & i_{(3)} & i_{(4)} & i_{(5)} & i_{(6)} \end{matrix}$

KCL: At any node, the algebraic sum of currents is 0.

$$\text{KCL (Node 2)} : i_{(2)} + i_{(4)} - i_{(5)} = 0$$

KCL equations in Graph Theory (GT)

$$A \cdot i = 0$$

i = column vector containing branch currents

$$A I(s) = 0$$

[KCL in Laplace domain in GT]

$$A = [A_t \quad A_l]$$

$$i' = \begin{bmatrix} i_t \\ i_l \end{bmatrix} \begin{array}{l} \text{Branch currents (tree)} \\ \text{Branch currents (links)} \end{array}$$

KCL:


$$[A_t \quad A_l] \begin{bmatrix} i_t \\ i_l \end{bmatrix} = 0$$

$$A_t \cdot i_t + A_l i_l = 0$$

$$i_t = -A_t^{-1} A_l i_l //$$

Nodal Analysis

[Figure out the node voltages]

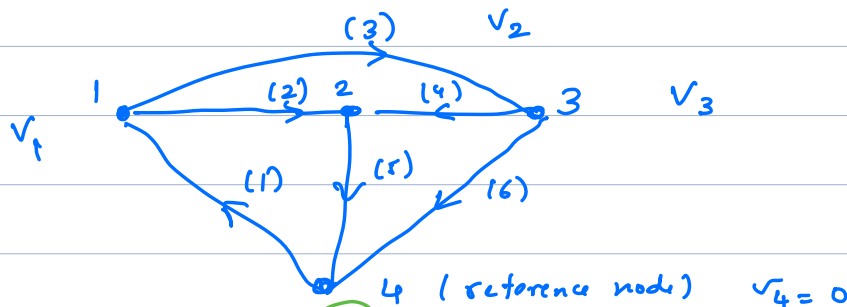

$$A = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 3 \end{matrix} & \begin{bmatrix} -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 0 & -1 & 1 & 0 \\ 0 & 0 & -1 & +1 & 0 & 1 \end{bmatrix} \end{matrix} \rightarrow \begin{pmatrix} v_1 \\ v_2 \\ v_3 \end{pmatrix}$$


$$\begin{matrix} v_n \\ \uparrow \text{ node voltage} \end{matrix} = \begin{pmatrix} v_1 \\ v_2 \\ v_3 \end{pmatrix} \quad \begin{array}{l} \text{Voltage across} \\ \text{branch (2)} \\ = v_1 - v_2 \end{array}$$

$$\begin{matrix} V \\ \text{(branch voltages)} \end{matrix} = A^T v_n$$

Example 17.4.1 in SK.

Case: Independent current sources



Independent voltage source
(cut-sets)

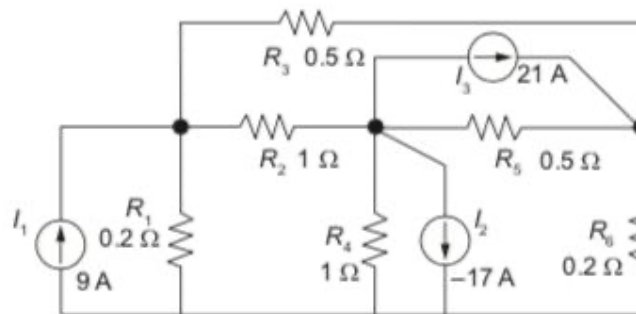

Step 1: Figure out the graph corresponding to this ckt

$A =$ Independent current sources

$y = \text{diag}(5, 1, \dots)$

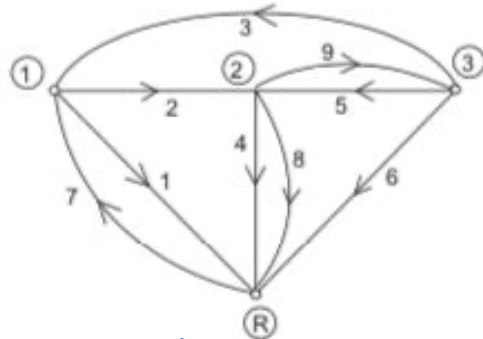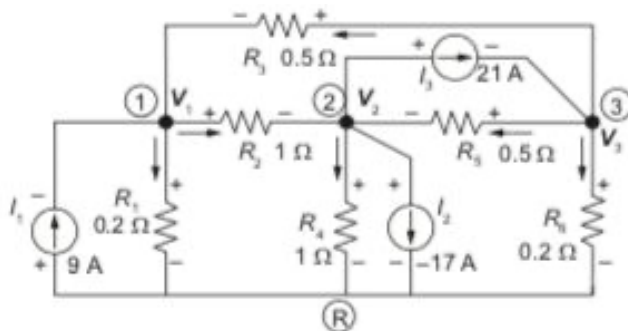

(1) (2) (3) (4) (5) (6) (7) (8) (9)

$$A = \left[\begin{array}{cccccc|ccc} 1 & 1 & -1 & 0 & 0 & 0 & -1 & 0 & 0 \\ 0 & -1 & 0 & 1 & -1 & 0 & 0 & 1 & 1 \\ 0 & 0 & 1 & 0 & 1 & 1 & 0 & 0 & -1 \end{array} \right]$$

A_p A_g

①

②

③

← Passive elements → ← Current source →

KCL equations: $A i = 0$

$$\begin{bmatrix} A_p & A_g \end{bmatrix} \begin{bmatrix} i_p \\ i_g \end{bmatrix} = 0$$

Is A_p invertible?

Known
 $i_g = \begin{bmatrix} 9 \\ 21 \\ -17 \end{bmatrix}$

Node voltages: $V_n = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$

$$V = A^T V_n$$

↑
branch voltages

$$\begin{bmatrix} V_p \\ V_g \end{bmatrix} = [A_p \ A_g]^T V_n$$

$$V_p = A_p^T V_n \quad \checkmark$$

R (Branch current) = Branch voltage

WL

1/jwc

For all passive elements:

$$\text{Branch current} = \text{Branch admittance} \times \text{Branch voltage.}$$

$$i_{(1)} = Y_1 V_1$$

$$i_{(2)} = Y_2 V_2$$

⋮

$$\begin{matrix} \nearrow \\ \text{branch} \\ \text{current} \\ \text{(passive)} \end{matrix} i_p = \begin{matrix} \vdots \\ Y \\ \vdots \end{matrix} V_p \quad \leftarrow \begin{matrix} \text{branch voltages} \\ \text{(passive)} \end{matrix}$$

$$Y = \text{diag}(Y_1, Y_2, \dots)$$

$$= \begin{bmatrix} Y_1 & & 0 \\ 0 & Y_2 & \\ & & \ddots \end{bmatrix}$$

$$[A_p \ A_g] \begin{bmatrix} i_p \end{bmatrix} = 0 \quad (\text{KCL})$$

$\begin{bmatrix} L & i_g \end{bmatrix}$

$$\begin{bmatrix} A_p & A_g \end{bmatrix} \begin{bmatrix} Y \cdot v_p \\ i_g \end{bmatrix} = 0$$

$$\begin{bmatrix} A_p & A_g \end{bmatrix} \begin{bmatrix} Y \cdot A_p^T v_n \\ i_g \end{bmatrix} = 0$$

$$A_p \underbrace{Y \cdot A_p^T}_{\text{Invertible}} v_n + A_g i_g = 0$$

$$v_n = - \underbrace{(A_p Y A_p^T)^{-1}}_{\text{Invertible}} A_g i_g$$

\hookrightarrow Equation for node voltages.

Exercise: Please work out for Example 17.4.1 in SK

$$(A_p Y A_p^T) - \text{Invertible? [Formal proof textbook]}$$

\swarrow \searrow \searrow
 $(n-1) \times p$ $p \times p$ $p \times (n-1)$

$$\text{rank}(A) = (n-1)$$