

Announcements: 1. Quiz 2 results released today

[Finish queries on Quiz by Sat (Nov 27)]

[Assume familiarity with everything taught in class]

2. Syllabus (B) for End Sem released today

3. Poll question results today. (5 out of 7)

4. End Sem: 15 marks (Part B) + Bonus

5. End sem logistics by Sat

✓ - Part B: Upload separately

[Similar to Test 2]

## Resonance

"High Q approximation"

General RLC  $\rightarrow$  Series RLC  
 $\rightarrow$  Parallel RLC



$\omega_0$ : Resonant freq:

$$Q_L = \frac{\omega L}{R}$$

Freq of interest: Around  $\omega_0$

$$Q_L \gg 1$$

$$> 10, > 5$$

$$Y_L(j\omega) = \frac{1}{R + j\omega L}$$

$$= \frac{R - j\omega L}{R^2 + \omega^2 L^2}$$

$$= \frac{R - j\omega L}{\omega^2 L^2 \left( 1 + \frac{R^2}{\omega^2 L^2} \right)}$$


$$\frac{\omega L - 1}{Q_L^2} < 0.01$$

$$\approx \frac{R - j\omega L}{\omega^2 L^2}$$


$$= \frac{R}{\omega^2 L^2} - \frac{j}{\omega L}$$

$$= \frac{1}{\left(\frac{\omega^2 L^2}{R^2}\right) R} + \frac{1}{j\omega L}$$

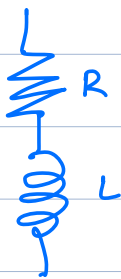
$$= \frac{1}{Q_L^2 R} + \frac{1}{j\omega L}$$



$Q_L \gg 1$   
 $\longleftrightarrow$

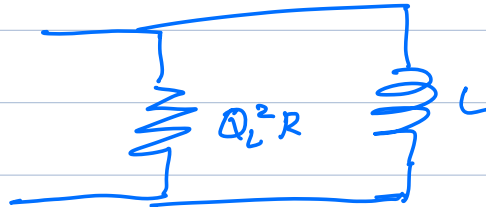

$\rightarrow$

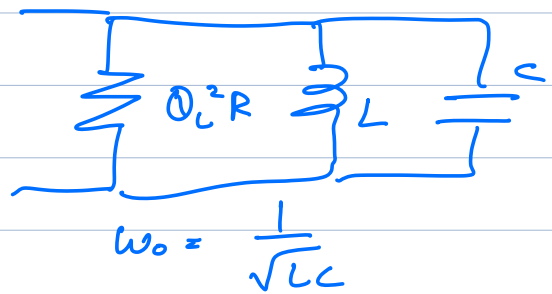


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Z_0(j\omega) = Q_L^2 R_L$$

"Impedance"  
at resonance


Example:

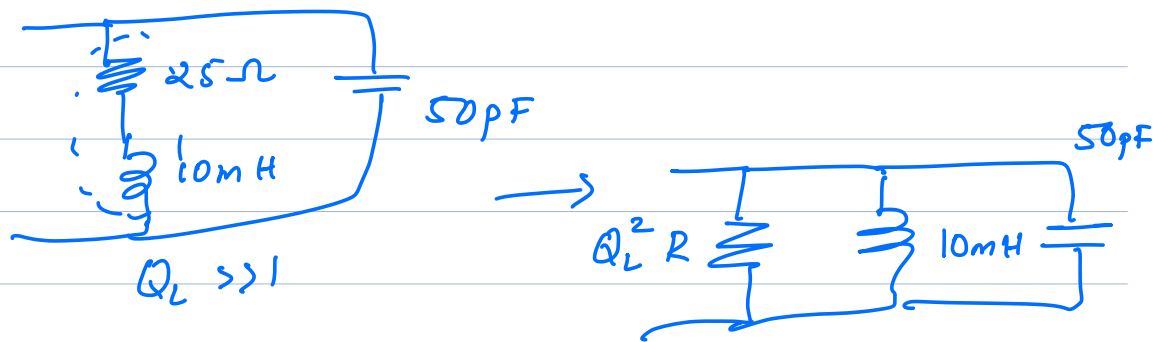

$$\omega_0 = \frac{1}{\sqrt{LC}} = \sqrt{2} \times 10^6$$

$$Q_L = \frac{\omega_0 \cdot L}{R} = \sqrt{2} \times 10^6 \times \frac{10\text{m}}{25} = \sqrt{2} \times 400 \gg 1$$


Generalization (Hayt) [ $Q \gg 1$ ]

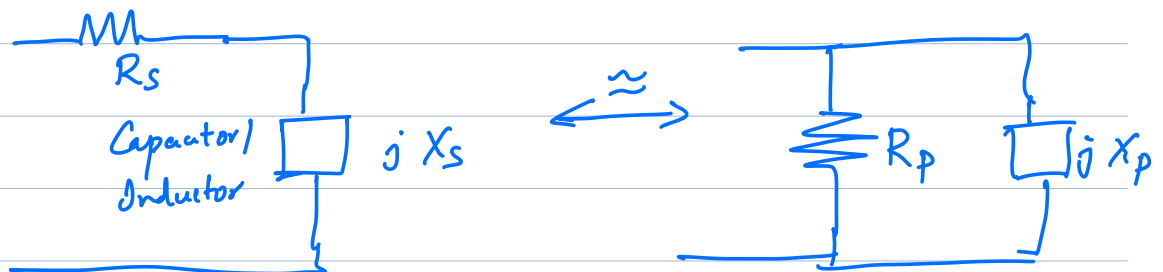


$$R_p = Q^2 \cdot R_s$$


$$X_p = X_s$$

Exercise:

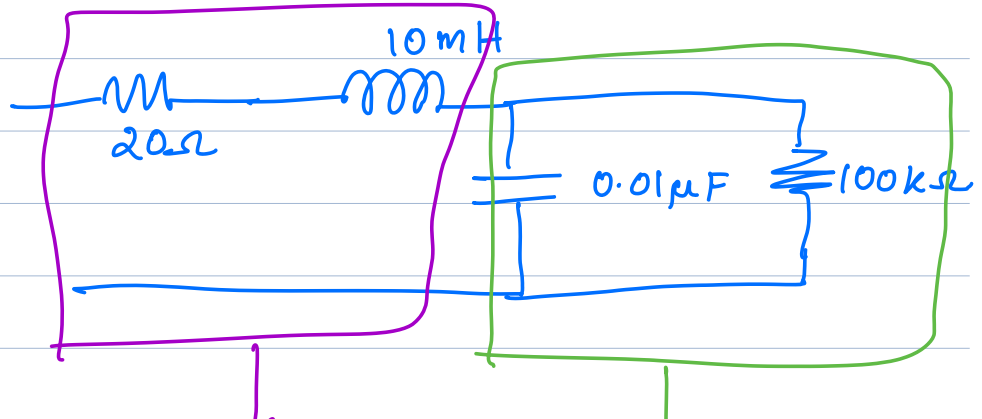

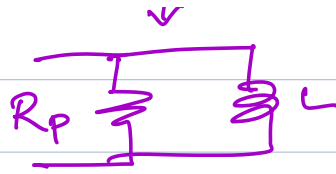

↓  
Parallel RLC

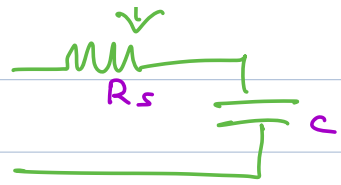

Series RLC

\_\_\_\_\_ X \_\_\_\_\_